


1.18

$$I_2 = 5\text{mA} \frac{(2.2\text{k}\Omega + 3.6\text{k}\Omega)}{(2.2\text{k}\Omega + 3.6\text{k}\Omega) + 4.7\text{k}\Omega} = 2.76 \text{ mA}$$

$$I_3 = 5\text{mA} \frac{4.7\text{k}\Omega}{5.8\text{k}\Omega + 4.7\text{k}\Omega} = 2.24 \text{ mA}$$

$$V_3 = 5\text{mA} (4.7\text{k}\Omega \parallel 5.8\text{k}\Omega) \frac{3.6\text{k}\Omega}{2.2\text{k}\Omega + 3.6\text{k}\Omega} = 8.06 \text{ V}$$

1.22

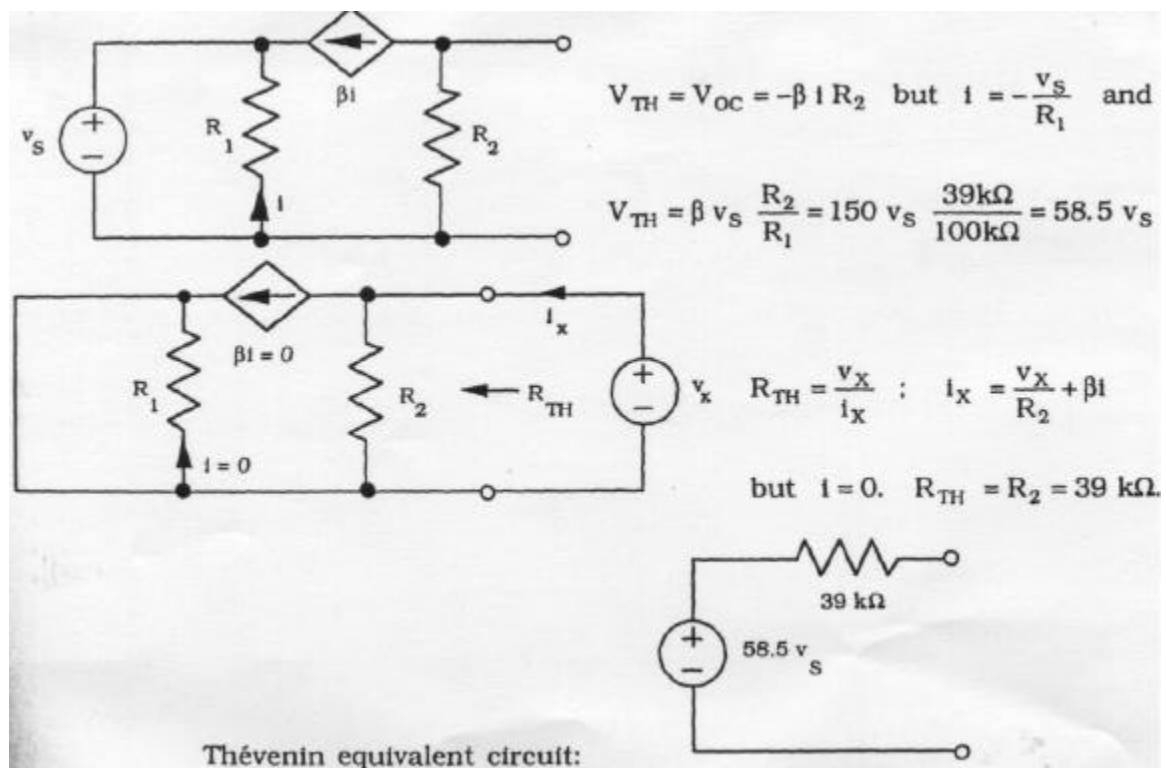

1.24

