

# A VHDL Synthesis Tutorial

First Edition

Valentina Salapura  
Michael Gschwind

Technische Universität Wien  
Vienna, AUSTRIA

© Copyright 1997 by V. Salapura and M. Gschwind

# Table of Contents

1. VHDL Primer
2. VHDL Simulation
3. Exercise 1: Simulation of an ALU
4. VHDL Synthesis Primer
5. Synthesis and Gate Level Simulation with Synopsys
6. Exercise 2: Synthesis of an ALU
7. Modeling Sequential Logic and Finite State Machines
8. Resource Sharing
9. Exercise 3: Design of a Digital Thermometer

For bug reports, please contact *valentina@vlsivie.tuwien.ac.at*

Disclaimer: the authors make no warranty of any kind with regard to this material, including, but not limited to, the implied warranties or merchantability and fitness for a particular purpose.

© Copyright 1997 by V. Salapura and M. Gschwind

All rights reserved. This book may be copied for non-commercial purposes. The material from this booklet may not be excerpted or stored in any other medium.

# VHDL Primer

Valentina Salapura  
Michael Gschwind

1-2

## About this VHDL primer

- ◆ **this is not a complete description of VHDL**
- ◆ **concepts have been simplified**
- ◆ **only issues and constructs related to synthesis are explained in this overview**
- ◆ **refer to a VHDL textbook for a full and exact description of the language**



## VHDL

- ◆ **VHSIC (Very High Speed Integrated Circuit) Hardware Description Language**
- ◆ **developed by DARPA Very High Speed IC Initiative sponsored by US Department of Defence**
- ◆ **IEEE standard hardware description language**
  - **IEEE Std. No. 1076 since 1988**
- ◆ **developed for design specification and validation**
- ◆ **required for government defence projects by DoD**
- ◆ **similar to ADA programming language**
  - **also developed by DoD**



© Copyright 1997 by V. Salapura & M. Gschwind

## VHDL references


- ◆ **The VHDL Cookbook, by Peter J. Ashenden**
  - **available via FTP**
  - <ftp://ftp.vlsivie.tuwien.ac.at/pub/hdl/VHDL-Cookbook.tar.Z>**
- ◆ **Peter J. Ashenden**  
**The Designer's Guide to VHDL**  
**Morgan Kaufmann Publishers, Inc.**
- ◆ **IEEE Standard 1076-1987**  
**IEEE Standard VHDL Language Reference Manual**




© Copyright 1997 by V. Salapura & M. Gschwind
 
## VHDL descriptions

- ◆ a design can be described in VHDL at different abstraction levels: for the description at the behavioral level, register-transfer level and at the gate level
- ◆ appropriate for describing both hardware structure and behavior



 © Copyright 1997 by V. Salapura & M. Gschwind



## VHDL as a programming language ...

- ◆ several constructs in VHDL like in programming languages (not hardware specific)
- ◆ comments : two hypens --
- ◆ identifiers : letter {[underline] letter number}
 

```
ThisName = thisname /= This_Name /= ThisName
```
- ◆ numbers : integer and real, in bases 2 - 16
 

```
1234 33E2 0.5 12.5E-9
2#11011 2#110.01 16#abc2
```
- ◆ character constants : using single-quote marks 'Z' '1'
- ◆ string constants : using double-quote marks "1100"
- ◆ bit strings: B⇒2, O ⇒8, X ⇒16 B "101010" X "A6"

© Copyright 1997 by V. Salapura & M. Gschwind



## Data types

- ◆ data type has to be declared - VHDL strongly typed language
- ◆ data type specified using type definition  
`type identifier is type_definition`
- ◆ basic data types
  - scalar
    - » integer types
    - » floating point types
    - » physical types
    - » enumeration types
  - composite
    - » arrays
    - » records



## Scalar data types

- ◆ integer: integer values within a specified range  
`type small is range 0 to 100;`  
`type bit_index is range 31 downto 0;`
- ◆ floating point: real values within a specified range  
`type probability is range 0.0 to 1.0;`
- ◆ physical: for physical quantities (mass, voltage, time...)  
`25 ns, 10 mm`
- ◆ enumeration: possible values are listed  
`type boolean is (true, false)`  
`type weekend is (sa, so)`



## Composite data types - arrays

◆ **array: indexed set of elements of the same type**

– one-dimensional and multidimensional

– constrained and unconstrained

– **example: one-dimensional, constrained**

```
type word is array (31 downto 0) of bit;
```

– **example: multidimensional, constrained**

```
type register_bank is array (0 to 31) of
word;
```

– **example: one-dimensional, unconstrained**

```
type word is array (positive range <>) of
bit;
```



## Composite data types - records

◆ **record: set of elements of different types**

```
type instruction is record
```

```
  op_code: processor_op;
```

```
  operand1: integer range 0 to 15;
```

```
  operand2: integer range 0 to 15;
```

```
end record;
```



## Subtypes

- ◆ constrained subset of some data type
- ◆ subtypes of scalar types and arrays
- ◆ examples:

```
type days is (mo, tu, we, th, fr, sa,
so);
```

```
subtype weekend is days range sa to so;
```

```
type bin_vector is array (integer range
<>) of bit;
```

```
subtype word is bin_vector(31 downto 0);
```



## Objects

- ◆ object: named item having value of a specified type
- ◆ three classes of objects

- constants

- variables

- signals

```
constant crc_pol: bit_vector(7 downto 0)
:= "00110011";
```

```
variable crc_acc: bit_vector(7 downto 0)
:= "11000011";
```

```
signal crc_reg: bit_vector(7 downto 0);
```



## Operators

- ◆ **logic operators**  
     **and, nand, or, nor, xor, not**
- ◆ **arithmetic operators**  
     **+, -, \*, /, \*\*, abs, mod**
- ◆ **relational operators**  
     **=, /=, <, <=, >, >=**
- ◆ **concatenation operator**  
     **&**



## Execution in VHDL

- ◆ **statements in VHDL can be executed sequentially and concurrently**
- ◆ **sequential statements only contained in processes**  
     – detailed explanation later, see **PROCESS** statement
- ◆ **several statements can be executed both sequentially and concurrently**
- ◆ **statements which can be executed both sequentially and concurrently**  
     – **signal assignment**  
     – **procedure call statement**



## Sequential and concurrent execution

- ◆ **statements executed sequentially:**
  - variable assignment
  - IF statement
  - CASE statement
  - LOOP statement
  - NULL statement
- ◆ **statements executed concurrently:**
  - PROCESS statement
  - conditional signal assignment
  - selected signal assignment
  - component instantiation statement



## Assignments and NULL statement

- ◆ **variable assignment**
  - sequential statement

```
a := new_value;    -- a is variable
```
- ◆ **signal assignment**
  - can be executed both sequentially and concurrently

```
b <= new_value;    -- b is signal
```
- ◆ **NULL statement**

```
null;
```



## IF statement

### ◆ IF statement

```
if condition_1 then
    sequence_of_statements
elsif condition_2 then
    sequence_of_statements
else
    sequence_of_statements
end if;
```



## CASE statement

### ◆ CASE statement

```
case expression is
    when choice_1 =>
        sequence_of_statements
    when choice_2 =>
        sequence_of_statements
    when others =>
        sequence_of_statements
end case;
```



## LOOP statement

- ◆ infinite loop

```
label: loop
    sequence_of_statements
end loop;
```

- ◆ basic loop statement can be extended to while or for loop

```
label: while condition | for parameter
    loop
    sequence_of_statements
end loop;
```

- ◆ NEXT and EXIT expressions optional

- NEXT: starts the next loop iteration
- EXIT: exits the loop



## Examples of LOOP statement

- ◆ while loop

```
Loop_1: while indx < max loop
    indx := indx + 1;
end loop;
```

- ◆ for loop

```
Loop_2: for indx in 1 to max loop
    vector_a(indx) <= '0';
end loop;
```



## Subprograms

- ◆ two forms
  - procedures
  - functions
- ◆ defined in two parts
  - declaration
    - » interface
  - body
    - » implementation
- ◆ statements in a subprogram are executed sequentially



## Subprogram declaration

- ◆ declaration syntax
  - procedure
 

```
procedure name (formal_parameter_list);];
```
  - function
 

```
function name [(formal_parameter_list)]
return type_result;
```
- ◆ declaration example
  - procedure
 

```
procedure read (L: inout line;
                 value: out std_logic);
```
  - function
 

```
function shl (arg: signed; count: unsigned)
return signed;
```



## Subprogram body

◆ **syntax**

```
subprogram_specification is
    subprogram_declarative_part
begin
    subprogram_statements_part
end name;
```



## Example: function body

```
function max (L, R: integer)
    return integer is
begin
    if L > R then
        return L;
    else
        return R;
    end if;
end max;
```



## Calling of subprograms

- ◆ if calling subprograms, parameters may be passed through
  - parameter position
 

```
read (act_line; new_value);
```
  - parameter name
 

```
read (value => new_value;
      L => act_line);
```
- ◆ overloading - several subprograms with the same name
  - subprogram is selected using the number and type of parameters



## Package

- ◆ encapsulated modules for structured programming
- ◆ collection of data types, constants, and subprograms
- ◆ defined in two parts
  - package declaration
    - » interface description
  - package body
    - » implementation
- ◆ package usage
 

```
use package_name.all;
use std_logic_1164.all;
```



## Package declaration

- ◆ syntax

```
package identifier is
  package_declarative_part
end identifier;
```

- ◆ example

```
package std_logic_1164 is
  type std_logic is ('U', 'X', '0', '1',
                    'Z', 'W', 'L', 'H', '-');
  type std_logic_vector is array
    (natural range <>) of std_logic;
  function "and" (L, R: std_logic_vector)
    return std_logic_vector;
  ...
end std_logic_1164;
```



## Package body


- ◆ contains subprograms implementations

- ◆ syntax

```
package body name is
  package_body_declaration_part
end name;
```

- ◆ example
 
```
package body std_logic_1164 is
  function "and" (L, R: std_logic_vector)
    return std_logic_vector is
  begin
  end "and";
  ...
end std_logic_1164;
```



## VHDL description of a function block

- ◆ consists of
  - entity
    - » description of the function block interface
    - » contains generics and ports
  - architecture body
    - » implementation of the block functionality
    - » multiple architecture bodies for same interface can be defined
      - ◆ different performance
      - ◆ different size
      - ◆ different abstraction levels
      - ◆ different detail
      - ◆ for simulation or for synthesis



## Entity declaration

- ◆ ports
  - input, output, inout
- ◆ generics
  - parameterize function blocks
  - select templates parameters
    - » delay (gates, ...)
    - » bit width (RAM, ALU, adder, ...)
    - » implementation (multiplier, divider, ...)
- ◆ syntax
 

```
entity identifier is
  generic (generics_constants_list);
  port (port_list);
end identifier;
```



## Example: entity declaration

```

entity processor is
  generic (width: integer);
  port(clock: in    std_logic;
        address: in  std_logic_vector(31 downto 0);
        data: inout std_logic_vector(31 downto 0);
        control: in  std_logic_vector(5 downto 0);
        ready: out  std_logic);
end processor;

```



## Architecture body

- ◆ contains the implementation of the block functionality
- ◆ several architecture bodies may be specified for each entity
  - different implementations
- ◆ architecture bodies implemented at different abstraction levels
  - structural
    - » block diagrams, net lists
  - RTL
    - » operation description using formulas
  - behavioral
    - » procedural description



## Architecture body syntax

- ◆ **syntax**

```

architecture identifier of entity_name
is
    architecture_declarative_part
begin
    architecture_statements_part
end identifier;
  
```



## Structural description

- ◆ **block functionality described as interconnection of smaller and simpler components**
  - net list, schematic
- ◆ **hierarchical block structure**
- ◆ **contains**
  - **components**
    - » function blocks, usage of existing design entities
  - **signals**
    - » for interconnection of components
- ◆ **advantage: easily mapped on hardware**
- ◆ **disadvantage: bad readability and overview**



## Components

- ◆ for structural descriptions, interconnected with signals
- ◆ existing entities used as components
- ◆ component described at different abstraction levels
  - different levels of detail
- ◆ component used in a structural description has to be
  - declared
    - » in the architecture body declaration part
  - instantiated
    - » in the architecture body statements part



## Component declaration

- ◆ in architecture body declaration part
- ◆ syntax
 

```
component identifier is
  generic(generic_constants_list);
  port(port_list);
end component;
```
- ◆ example
 

```
component counter
  generic(N: integer);
  port(clock, reset: in std_logic;
        y: out std_logic_vector(0 to N-1));
end component;
```



## Component instantiation

- ◆ in architecture body statements part
- ◆ specify connections and parameters for generic parameterizable modules
- ◆ syntax

```
label: name generic map (generic_list);
      port map (port_list);
```

- ◆ example

```
u3: counter generic map (4);
      port map (clk, n245, n254);
```


parameter for  
parameterizable blocks

connections


 
## Structural description - example

- ◆ multiply-and-accumulate function block
- ◆ block diagram



## MACC Entity

```

entity macc is
  port(
    in1:    in  std_logic_vector(7 downto 0);
    in2:    in  std_logic_vector(7 downto 0);
    clock:  in  std_logic;
    result: out std_logic_vector(15 downto 0));
end macc;

```



© Copyright 1997 by V. Salapura & M. Gschwind

## Architecture body - structural description

```

architecture structure of macc is
  signal mul_res: std_logic_vector(15 downto 0);
  component mult
    port(a,b: in  std_logic_vector(7 downto 0);
        y:    out std_logic_vector(15 downto 0));
  end component;
  component acc
    port(a:    in  std_logic_vector(15 downto 0);
        clk:   in  std_logic;
        y:    out std_logic_vector(15 downto 0));
  end component;
  begin
    multiply: mult port map(in1, in2, mul_res);
    accum:    acc  port map(mul_res, clock, result);
  end structure;

```



© Copyright 1997 by V. Salapura & M. Gschwind

## RTL description

- ◆ register transfer level
- ◆ description at higher abstraction level
- ◆ operations described with formulae
- ◆ usage of signals
  - for value exchange between formulae
- ◆ functionality described as calculation of new signal value from other signals
 
$$y_n = f(y_k, y_l, \dots)$$
- ◆ advantage: good readability
- ◆ disadvantage: complicated mapping on hardware



## Simplified VHDL simulation model

- ◆ execution of a VHDL description
  - statements in an endless loop
  - all statements executed repeatedly
  - signal change visible only in the next simulation loop iteration
    - » signals introduce one unit delay
    - » abstract model of hardware delay



## Consequences of signal delay


- ◆ in architecture body all statements executed concurrently
  - corresponds to hardware where all components and wires concurrently active
- ◆ order of concurrent statements not important
- ◆ exact delay of signals possible using “after” clause



© Copyright 1997 by V. Salapura & M. Gschwind
 
## Execution of concurrent statements

- ◆ exercise:
  - write an RTL description for the following block diagram



© Copyright 1997 by V. Salapura & M. Gschwind

## Solution

```

entity simple is
    port(a,b:      in  std_logic;
          y1,y2,y3: out std_logic);
end simple;

architecture arch of simple is
begin
    y2 <= a and not(b);
    y1 <= not(a) and b;
    y3 <= a or (not(a) and b);
end arch;

```



## AFTER clause

- ◆ defines exact delay
- ◆ syntax
 

```

target <= value_expression after
                    time_expression;

```
- ◆ example
 

```

out2 <= not(in2) after 5 ns;
in2  <= out1 after 1 ns;

```



## Concurrent statements

- ◆ signal assignment
- ◆ conditional signal assignment
  - corresponds to sequential IF
- ◆ selected signal assignment
  - corresponds to sequential CASE



## Conditional signal assignments

- ◆ concurrent IF
- ◆ syntax
 

```
target <= {waveform when condition else}
          waveform;
```
- ◆ example
 

```
reset <= '0', '1' after 10 ns when
          short = '1' else
          '0', '1' after 25 ns;
```



## Selected signal assignment

- ◆ concurrent CASE

- ◆ syntax

```
with expression select
    target <= {waveform when choice,}
             waveform when choice;
```

- ◆ example

```
with code select
    result <= a + b when addition,
             a - b when subtract;
```



## MACC - RTL Description

```
architecture rtl of macc is
    signal mul_res,reg: std_logic_vector(15
        downto 0);
    begin
        reg <= reg + in1 * in2 when
            clock = '1' and clock'event;
        result <= reg;
    end rtl;
```

rising clock edge

 A small timing diagram is shown to the right of the code. It consists of a horizontal line representing a clock signal. An arrow points to the first rising edge of the signal, which is labeled 'rising clock edge'. The text 'clock = '1' and clock'event;' from the code is circled in grey, and an arrow points from this circled text to the rising edge in the diagram.

- ◆ VHDL defines attributes for various object types

- for signals: ' event - signal value has changed



## Behavioral description

- ◆ descriptions at high abstraction level
- ◆ behavioral VHDL similar to “normal” programming languages
- ◆ encapsulated in VHDL processes
- ◆ advantages
  - simple and quick description
  - high simulation speed
- ◆ disadvantages
  - complicated mapping on hardware
  - less detailed description



## Process statement

- ◆ concurrent statement in architecture body
  - executed concurrently with other statements
- ◆ contains sequential statements
  - encapsulated statements executed sequentially
- ◆ variables used in a process
  - variables change value immediately, like in “normal” programming languages
- ◆ signals can still be used
  - semantics differ from variable  $\Rightarrow$  changes only visible in next iteration of process
  - useful for communication with other concurrent elements in architecture body



## Process statement: syntax

```
process [(sensitivity_list)]  
    process_declarative_part  
begin  
    process_statements_part  
end process;
```



## Process statement: example

```
P22: process (clock, reset)  
    begin  
        if reset = '1' then  
            reg <= "0000";  
        elsif clock = '1' and clock'event then  
            reg <= "1100";  
        end if;  
    end process;
```



## Building a VHDL description

- ◆ in a single VHDL design used many different packages, architecture bodies and entities
- ◆ active components (architecture bodies, packages) for a particular design selected using
  - libraries
  - configurations



## Library

- ◆ encapsulates various related components
- ◆ identified with a logic name
- ◆ design descriptions compiled in libraries for simulation and synthesis
- ◆ order of compilation important
  - primary library units
    - » have to be compiled first
    - » package declarations, entities, configuration declaration
  - secondary library units
    - » package bodies, architecture bodies



## Using libraries

- ◆ referenced with “use” clause
- ◆ example
 

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
```
- ◆ library “work” always selected
  - working library
  - need not to be referenced



## Configuration

- ◆ configuration selects
  - architecture body for entities
  - entities for components
  - generics for components
- ◆ selects architecture body for each instance, e.g.
  - architecture body with optimized timing for timing critical parts
  - architecture body with minimal area for area critical parts
  - behavioral description for fast simulation



## Configuration syntax

```

configuration identifier of entity_name
is
  use_clause
  for architecture_name
    use_clause
    for block_name ...
    end for;
  end for;
end identifier;

```

- ◆ first hierarchical “for” clause specifies architecture body



## Configuration: example

```

architecture simulate of adder is
  component hadd port(...); end component;
begin
  B1: hadd port map(...);
  B2: hadd port map(...);
end simulate;

configuration mixed of adder is
  for simulate
    for B1:
      hadd use entity work.hadd(rtl); end for;
    for B2:
      hadd use entity work.hadd(synth); end for;
    end for;
  end mixed;

```



## Standard logic

- ◆ standardized data types for portably describing signal values in VHDL
- ◆ IEEE standard multivalued logic system for VHDL model interoperability (Std\_logic\_1164)
  - IEEE Std. No. 1164-1993
  - defined in `IEEE.std_logic_1164` package
- ◆ should be supported by all simulators and synthesis tools
- ◆ simple mapping on hardware
- ◆ arithmetic operations on `std_logic` standardized in IEEE 1076.3 synthesis package `Numeric_Std`



## Standard logic data types

- ◆ data type `std_logic`:
  - 'U' - not initialized
  - 'X' - unknown, strong
  - '0' - 0, strong
  - '1' - 1, strong
  - 'Z' - high impedance (tri-state)
  - 'W' - unknown, weak
  - 'L' - 0, weak
  - 'H' - 1, weak
  - '-' - don't care



## Other standard data types

- ◆ `std_logic_vector`
- ◆ `std_ulogic, std_ulogic_vector`
  - unresolved `std_logic`
    - » several drivers drive single bus / wire
- ◆ `signed, unsigned`
  - defined in IEEE 1076.3 Numeric\_Std
  - array of `std_logic` with integer semantics



## Data type conversion functions

- ◆ VHDL strongly typed - but not hardware
  - synthesis tools have to provide trivial mapping of functions
- ◆ in synthesis package `IEEE.std_logic_arith`
- ◆ most important conversion functions
  - `conv_integer`
  - `conv_unsigned`
  - `conv_signed`
  - `conv_std_logic_vector`



## Some conversion functions

- ◆ `conv_integer`
  - input is `integer | signed | unsigned | std_logic`
  - return `integer`
- ◆ `conv_unsigned, conv_signed`
  - input is `integer | signed | unsigned | std_logic`
  - return `unsigned, signed`
- ◆ `conv_std_logic_vector`
  - input is `integer | unsigned | signed | std_logic`
  - parameter `integer` (for width)
  - return `std_logic_vector`



# VHDL Simulation

Valentina Salapura  
Michael Gschwind

2-2

## Introductory note

- ◆ this collection only gives short overview of simulation
- ◆ concepts have been simplified
- ◆ intended to give basic understanding of VHDL simulation
- ◆ for full information on VHDL simulation check VHDL simulation text book



## Simulation

- ◆ for validating VHDL Models
- ◆ simulation shows
  - whether errors are found for given test vectors
  - not that the design is correct
- ◆ quality of test vectors is critical for quality of simulation



## Simulation development

- ◆ 1980 - CAE
  - simulation at the gate level
    - » long simulation time
- ◆ 1990 - High level approach
  - simulation at behavioral and RTL levels
    - » usage of test benches
    - » procedural description of test vectors
    - » simple and quick design at higher abstraction level
    - » faster simulation because less detail required



## Usage of simulation

- ◆ **VHDL system simulation**
  - behavioral and RTL description
- ◆ **post-synthesis simulation and timing analysis**
  - at the gate level
- ◆ **sign-off simulation**
  - after layout and routing
    - » exact timing analysis



## Simulation model

- ◆ **discrete event simulation**
- ◆ **simulation controlled by events  $\Rightarrow$  event driven simulation**
  - event – the value of a signal had changed
  - change of a signal is not immediately executed
  - assignment of new signal values scheduled along a time axis



## Simulation algorithm


- ◆ defined by IEEE VHDL standard 1076
- ◆ simulation starts with the initialization phase
  - simulation time = 0
  - all objects initialized
- ◆ iterate 2 stage simulation cycle
  - propagation
    - » all transactions (signal changes) scheduled for this simulation time executed
  - evaluation
    - » execute all VHDL modules which react to events occurring in the first stage
    - » schedule new signal changes



© Copyright 1997 by V. Salapura & M. Gschwind

## Delta method

- ◆ two dimensional time

 

- ◆ guarantees
  - compatibility between different simulators
  - determinism




© Copyright 1997 by V. Salapura & M. Gschwind
 
## Signal assignment

- ◆ without “after” clause
- ◆ input a is '0' at t0

```
architecture simple of demo is
begin
  b <= a;
  c <= not(b);
end simple;
```




© Copyright 1997 by V. Salapura & M. Gschwind


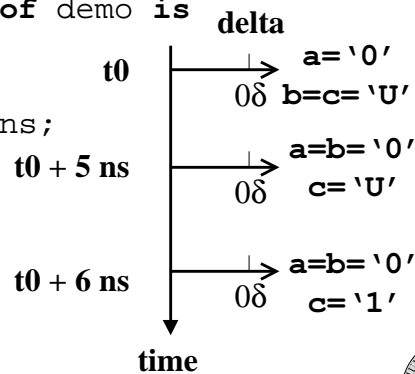
## Signal assignment (2)

- ◆ with “after” clause
- ◆ input a is '0' at t0

```
architecture simple of demo is
begin
  b <= a after 5 ns;
  c <= not(b) after 1 ns;
end simple;
```



© Copyright 1997 by V. Salapura & M. Gschwind



## Controlling simulation

- ◆ **evaluate**
  - only the modules affected by changed signals
    - » activation list for concurrent statements
    - » sensitivity list for processes
- ◆ **propagate**
  - only the signals whose value should change



## VHDL for simulation

- ◆ **statements for describing time flow in the simulation**
  - **after**
    - » for time flow of signal assignments
 


```
a <= "11110000" after 100 ns;
```
  - **wait**
    - » to start and stop a process
 

```
wait for 10 ns;
wait until reset = '1';
wait on clock'event;
```


 
## Test bench

- ◆ defines the stimuli of a design
- ◆ consists of two components
  - UUT (unit under test)
    - » tested design
  - TG (test generator)
    - » generates stimulus for the design
    - » collects the design's response, compares with reference values




© Copyright 1997 by V. Salapura & M. Gschwind


 
## Types of test bench

- ◆ system test bench
  - describes the design environment
  - designer know how
- ◆ comparison test bench
  - compares the implementation with a reference model
    - » reference model = expected simulation results at higher abstraction levels or golden device
    - » difficulties with timing differences between the implementation and the reference model



© Copyright 1997 by V. Salapura & M. Gschwind



## Building a test bench

```

entity TB is
end TB;

architecture TBA of TB is
    declarative_part_signals_components
begin
    instantiate_UUT_and_other_components
    and_optional
    behavioral_description_of_TG
end TBA;
  
```



© Copyright 1997 by V. Salapura & M. Gschwind

## Putting together a simulation model

- ◆ **arranging a configuration**
  - **connecting objects**
    - » **component** <=> **entity**
    - » **entity** <=> **architecture**
    - » **generics**
- ◆ **example**

```

configuration cfg_tb of TB is
  for TBA:
    for uut: u_entity
      use entity work.u_entity(u_arch);
    end for;
  end for;
end cfg_tb;
  
```



© Copyright 1997 by V. Salapura & M. Gschwind

## Simulation of VHDL models

- ◆ VHDL model has to be
  - compiled (analyzed)
  - simulated
- ◆ simulation using Synopsys
  - interpreted
    - » intermediate format (byte code)
    - » similar to VHDL source code
    - » easy debugging
    - » slow simulation
  - compiled
    - » translated to machine code
    - » fast simulation



## Working environment for Synopsys

- ◆ setup file in the working directory
  - `.synopsys_vss.setup`
    - contains data path for system libraries
- ◆ library work
  - contains analyzed elements
- ◆ typical working directory - listing
 

```
ls
  .synopsys_vss.setup  # Synopsys configuration
  vhdl_file.vhd       # VHDL source file
  work/               # contains analyzed source
```
- ◆ Synopsys online documentation
  - `iview`



## Compilation with Synopsys

- ◆ compilation command (for library work)
 

```
vhdlan vhd1_file.vhd
```
- ◆ compilation to other libraries
 


```
vhdlan vhd1_file.vhd -w library_name
```

– library name has to be specified in  
`.synopsys_vss.setup`


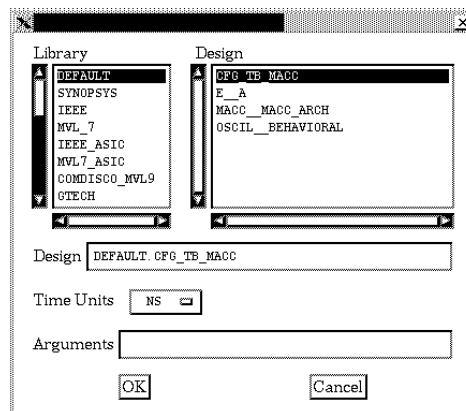
## Simulation with Synopsys

- ◆ Synopsys VHDL debugger - `vhdlbxx`
- ◆ select design



## Useful commands

- ◆ **trace**
  - signal selection for waveforms
- ◆ **cd**
  - moving through the program hierarchy
- ◆ **step, next**
  - execute simulation in steps
- ◆ **run *time\_expression***
  - simulation start
- ◆ **include**
  - usage of scripts



## Vhdlldb - working window

The screenshot shows a window titled "Execute Breakpoints Monitors Traces Query Stimulus Misc". The main text area contains the following VHDL code:

```

12 ARCHITECTURE macc_arch OF macc IS
13
14 SIGNAL new_val, reg : integer range 0 to 65535;
15
16 BEGIN
17
18   >Regis: PROCESS(clock, reset)
19     BEGIN
20       IF reset = 1 THEN
21         reg <= 0;
22       ELSIF clock'EVENT and clock = 1 THEN
23         reg <= new_val;
24       <--END IF;
25     END PROCESS;
26
27     new_val <= reg + input1 * input2 after 15 ns;
28

```

Below the code, the window shows:

```

UWR : /TB/UUT/REGIS                               File: macc_int.vhd
Time : 100 NS                                       Line: 18

```

A toolbar contains buttons: Stop at, Clear, Trace, Event Bkpt., Eval., Step, Next, Intr., Ed, Run, and a text input field.

The bottom text area contains the following commands:


```

# trace in1 in2 res clock result
# cd uut
# trace new_val reg
# run 100
100 NS
#

```



## Vhdlbx - waveforms

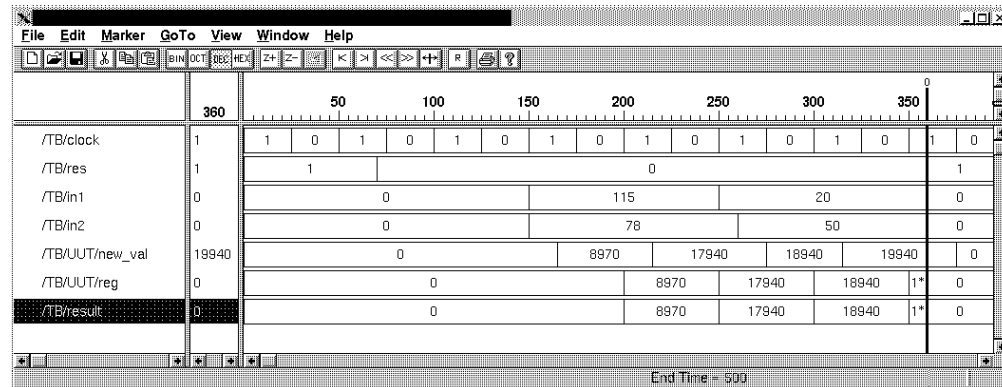

© Copyright 1997 by V. Salapura & M. Gschwind



## Simulation example: MACC entity

```

use work.all;
ENTITY macc IS
  PORT (
    input1: IN   integer range 0 to 255;
    input2: IN   integer range 0 to 255;
    reset:  IN   integer range 0 to 1;
    clock:  IN   integer range 0 to 1;
    out_reg: OUT integer range 0 to 65535
  );
END macc;

```

© Copyright 1997 by V. Salapura & M. Gschwind



## Simulation example: MACC architecture

2-25

```
ARCHITECTURE macc_arch OF macc IS
  SIGNAL new_val, reg: integer range 0 to 65535;
BEGIN
  Regist: PROCESS(clock, reset)
  BEGIN
    IF reset = 1 THEN
      reg <= 0;
    ELSIF clock'EVENT and clock = 1 THEN
      reg <= new_val;
    END IF;
  END PROCESS;
  new_val <= reg + input1 * input2 after 15 ns;
  out_reg <= reg;
END macc_arch;
```

© Copyright 1997 by V. Salapura & M. Gschwind



## Simulation example: Oscillator for clock signal

2-26

```
ENTITY oscil IS
  PORT(txc: OUT integer range 0 to 1:=0);
END oscil;
ARCHITECTURE behavioral OF oscil IS
BEGIN
  PROCESS
  BEGIN
    LOOP
      txc <= 1;
      wait for 25 ns;
      txc <= 0;
      wait for 25 ns;
    END LOOP;
  END PROCESS;
END behavioral;
```

© Copyright 1997 by V. Salapura & M. Gschwind



## Simulation example: MACC test bench

```

entity TB is
end TB;

Architecture Arch of TB is
  SIGNAL in1, in2: integer range 0 to 255;
  SIGNAL res, clock: integer range 0 to 1;
  SIGNAL result: integer range 0 to 65535;

  COMPONENT macc
    PORT (input1, input2: IN integer range 0 to 255;
          reset, clock: IN integer range 0 to 1;
          = out_reg: OUT integer range 0 to 65535);
  END COMPONENT;

  COMPONENT oscil
    Port (txc: OUT integer range 0 to 1);
  END COMPONENT;
%
```

© Copyright 1997 by V. Salapura & M. Gschwind



## Simulation example: MACC test bench

cont'd

```

BEGIN

UUT : macc PORT MAP (in1, in2, res, clock, result);
clk : oscil PORT MAP (clock);

TBP : PROCESS
  BEGIN
    in1 <= 0; in2 <= 0; res<=1;
    wait for 70 ns; -- reset cycle
    res<=0; wait for 80 ns;
    in1 <= 115; in2 <= 78; -- input data
    wait for 100 ns;
    in1 <= 20;= -- new input data
    wait for 10 ns;
    in2 <= 50;
    wait for 100 ns;
  END PROCESS;
end Arch;
```

© Copyright 1997 by V. Salapura & M. Gschwind



## Simulation example: MACC configuration

```


configuration cfg_tb_macc of TB is
  for Arch:
    for uut: macc
      use entity work.macc(macc_arch);
    end for;
  end for;
end cfg_tb_macc;

```



© Copyright 1997 by V. Salapura & M. Gschwind
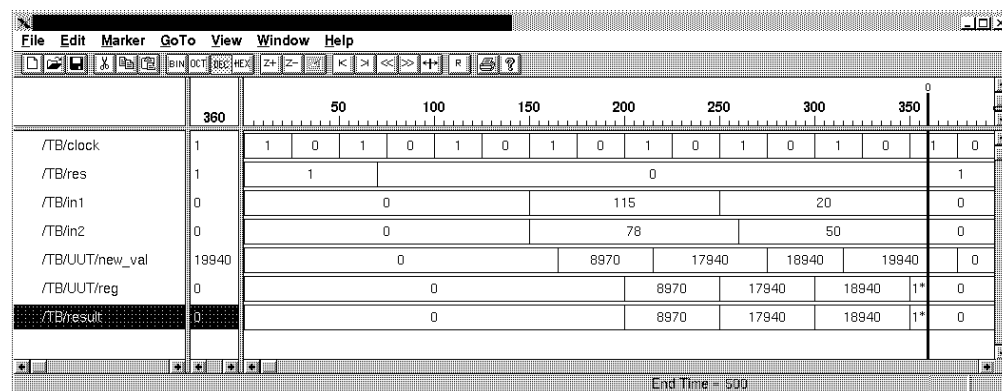
## Simulation example: Tracing MACC operation using waveforms



© Copyright 1997 by V. Salapura & M. Gschwind

# Exercise 1

## VHDL design and simulation

Valentina Salapura  
Michael Gschwind

E1-2

### ALU design and simulation

- ◆ describe an ALU with following properties in VHDL
  - 2 data inputs, 1 output
    - » data type integer range 0 to 256
  - control input for operation selection
    - » choose appropriate encoding for function selection: enumeration data type, integer, bitstring...
  - ALU operations

	<b>delay</b>
» pass A, pass B	2 ns
» not A, A and B, A or B, A xor B	5 ns
» A + B, A - B	16 ns
» A * B	50 ns



## Complete the following tasks

- ◆ describe the ALU in VHDL
- ◆ develop a test bench for simulation
- ◆ verify ALU functionality using functional simulation
- ◆ explain your design decisions and their impact



# VHDL Synthesis Primer

Valentina Salapura  
Michael Gschwind


3-2

## Synthesis

- ◆ **automatic translation from one abstraction level to a lower abstraction level**
  - generates more detailed descriptions
- ◆ **hardware structure directly inferred from an HDL description**
  - hardware not specified explicitly
  - ⇒ coding style important for efficiency




## Gajski's Y-Diagram

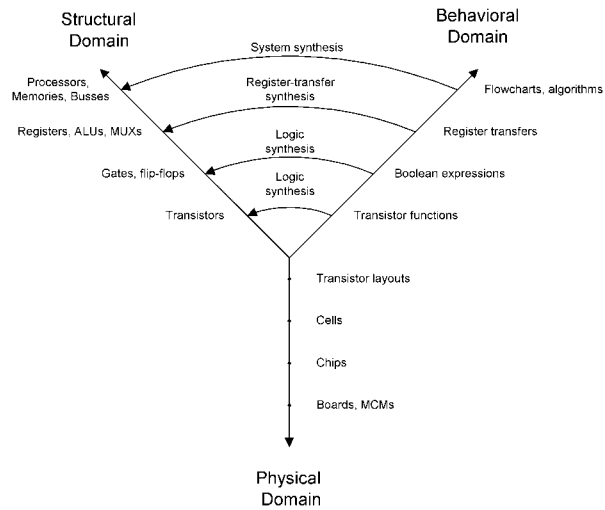

© Copyright 1997 by V. Salapura & M. Gschwind



## Design steps in Y-Diagram

 

© Copyright 1997 by V. Salapura & M. Gschwind



## Synthesis at different abstraction levels

- ◆ system level synthesis
- ◆ high-level synthesis
- ◆ RTL synthesis
- ◆ logic-level synthesis
- ◆ technology mapping



© Copyright 1997 by V. Salapura & M. Gschwind

## Theory ... synthesis at high abstraction levels

- ◆ system level synthesis
  - partitioning of a system into subsystems and definition of its algorithms
- ◆ behavioral synthesis (high-level synthesis)
  - translation from a behavioral into an RTL description
  - explore different architectures
  - design divided in data and control path (resource allocation, scheduling, resource assignment)



© Copyright 1997 by V. Salapura & M. Gschwind

## Theory ... RTL and logic synthesis

- ◆ **RTL synthesis**
  - performs control and data path synthesis
  - resource allocation and sharing
    - » maps RTL description to Boolean functions
- ◆ **logic-level synthesis**
  - design described with combinational logic (Boolean functions) and sequential elements
  - description mapped to the gate level and optimized



## Theory ... Technology mapping

- ◆ **technology mapping**
  - abstract gates mapped to technology elements
  - function blocks sometimes mapped to macros



## ... and reality

- ◆ **system synthesis does not exist**
- ◆ **behavioral synthesis - first tools available**
  - for example, Behavioral Compiler from Synopsys
- ◆ **RTL + logic synthesis available today**
  - in good tools no difference between these steps
  - for example, Design Compiler from Synopsys
- ◆ **pure logic synthesis**
  - available for a long time, e.g. Espresso
  - optimization of Boolean equations



## Advantages of synthesis

- ◆ **shorter design time**
- ◆ **simplifies modularity and simple integration of design**
- ◆ **management of design complexity**
  - 10M transistor designs already exist, and growing!
- ◆ **facilitates optimization of the whole design**
  - removal of redundant functions
- ◆ **enables simple porting of design to other technologies by re-synthesizing it**



## Intellectual property (IP) theory

- ◆ **how to make 100 Mgate designs**
  - buy already existing design blocks from IP vendors
    - » x86 VHDL model
    - » chip set model
    - » SCSI controller model
    - » Ethernet controller model
  - ⇒ equals PC on a chip
  - synthesize all blocks in a single chip
- ◆ **today's integration of components on printed circuits board ⇒ tomorrow's integration of hardware descriptions on a chip**



## Disadvantages of synthesis

- ◆ synthesized hardware depends on coding style
- ◆ synthesis efficiency depends on
  - synthesis tools used
  - target technology
  - ⇒ less portable than ideally possible
- ◆ less control over the resulting hardware
- ◆ hand design of particular blocks may be better than the synthesis result
  - but hand design probably depends on technology



## HDL - hardware description languages

- ◆ synthesis based on HDL
- ◆ most common HDLs: VHDL and Verilog
- ◆ developed for simulation, not for synthesis
  - synthesis semantics sometimes different from simulation semantics
  - what you synthesize is not always what you simulate
- ◆ synthesis basics similar for all HDLs



## Verilog

- ◆ mostly used in the US
- ◆ developed by Gateway Design Automation software company 1983
- ◆ similar to “C” programming language
- ◆ data types defined by language, not by user




## VHDL

- ◆ mostly used in Europe
- ◆ developed by DoD – required for defense contracts
- ◆ strong typing system
- ◆ similar to “ADA” – by design
  - also developed by DoD
  - usage of data types and libraries
  - similar syntax



© Copyright 1997 by V. Salapura & M. Gschwind

## Design flow

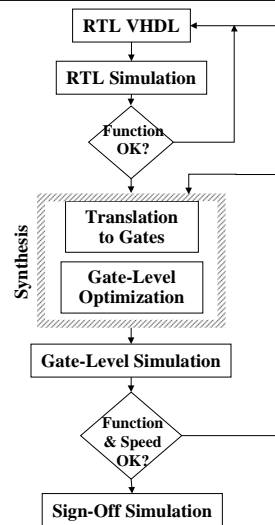

© Copyright 1997 by V. Salapura & M. Gschwind

## Synthesis tools

- ◆ RTL and logic synthesis widely used for approximately 5 years
- ◆ up to date hardware design method
- ◆ synthesis tools well developed, but quality of synthesis results varies
  - Synopsys, Compass, Powerview, Cadence, ...
- ◆ some synthesis tools ignore configuration specification and/or user-defined libraries
- ◆ some synthesis tools do not support resource-sharing



## Mapping HDL to hardware

- ◆ in an HDL description, hardware is not explicitly defined
- ◆ structure of hardware inferred from the structure of a HDL description
  - ⇒ the quality of synthesized hardware depends on coding style of an HDL description
    - possibly also depends on synthesis tools and target technology



## HDL translation for synthesis

- ◆ translation in two steps (as performed by Synopsys Design Compiler)
  - module generator - modules inferred from an HDL description
    - » modules for simple operations
    - » technology independent
  - module mapping to gates
    - » technology specific
    - » makes gate-level design optimization possible




## Synthesis environment

- ◆ VHDL based synthesis
- ◆ synthesis tools `design_analyzer` from Synopsys
  - probably the best synthesis tool currently available
- ◆ target technology (for our experiments) is the ASIC technology LSI 10K
  - available in the Synopsys standard distribution
  - 1.5 $\mu$ , double metal, single poly
    - » approximately 10 years old
  - technology library specified in file `.synopsys_dc.setup`



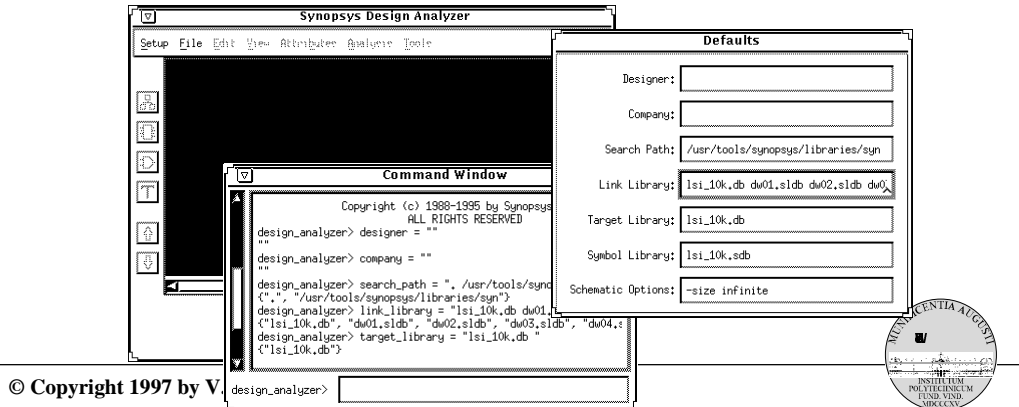
## Synthesis using Synopsys

- ◆ invoke `design_analyzer`
- ◆ `setup` ⇒ defaults – selected technology libraries  
⇒ command window – command line input


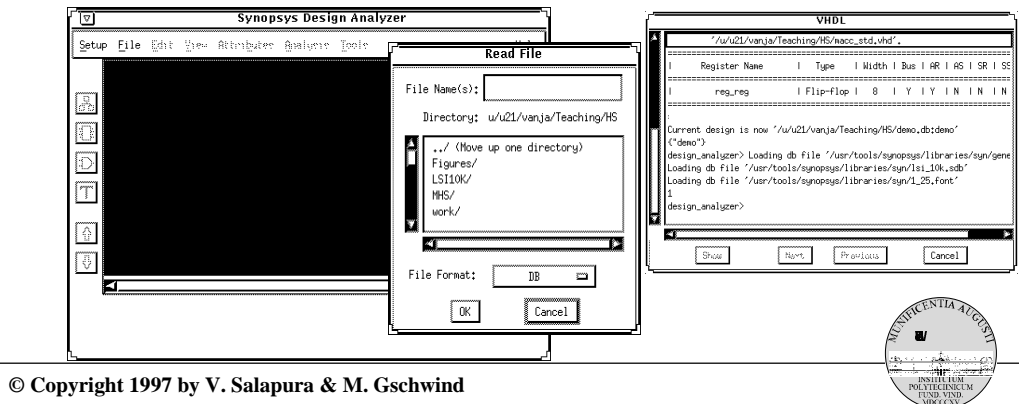
## Synthesis using Synopsys

- ◆ synthesis executed in two steps
- 1. step: `file` ⇒ `read` – read in VHDL files  
» macro for commands `analyze` and `elaborate`



## Mapping VHDL constructs

- ◆ synthesis tools map VHDL constructs to three hardware elements
  - combinational logic
  - multiplexors
  - memory elements
- ◆ what hardware is generated from
  - arithmetic, logic and comparison operators
  - IF and CASE statements
  - indexes and arrays
  - process statement



## Arithmetic and logic operations

- ◆ arithmetic and logic operation are mapped to combinational logic

```


LIBRARY IEEE, work;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
use work.all;
ENTITY adder IS
  PORT (A,B:  IN  std_logic_vector(3 downto 0);
        Y1,Y2: OUT std_logic_vector(3 downto 0));
END adder;
ARCHITECTURE arch OF adder IS
BEGIN
  Y1 <= A + B;
  Y2 <= A AND B;
END arch;

```


 
## Result of synthesis

- ◆ step 1: modules for simple operators
- ◆ step 2: tools  $\Rightarrow$  design optimization – modules mapped to gate level and optimized



© Copyright 1997 by V. Salapura & M. Gschwind





## Comparison operators

- ◆ comparison operators are mapped to combinational logic

```
ENTITY compare IS
  PORT (I1, I2: IN std_logic_vector
        (3 downto 0);
        Y1: OUT boolean);
END compare;
```
  
```
ARCHITECTURE arch OF compare IS
  BEGIN
    Y1 <= ( I1 < I2 );
  END arch;
```



© Copyright 1997 by V. Salapura & M. Gschwind



## Array indexes

### ◆ from a variable index - multiplexor

```


ENTITY indexing IS
  PORT(A: IN std_logic_vector
        (7 downto 0);
        Sel: IN integer range 0 to 7;
        Y: OUT std_logic);
END indexing;

```

```

ARCHITECTURE arch OF indexing IS
BEGIN
  Y <= A(Sel);
END arch;

```

 

### ◆ from a constant index - wire

```

Y <= A(3);

```



## IF statement

### ◆ IF statements are mapped to multiplexors

```



ENTITY muxing IS
  PORT(A,B: IN std_logic_vector
        (7 downto 0);
        Sel: IN std_logic;
        Y: OUT std_logic_vector
        (7 downto 0));
END muxing;

```

```

ARCHITECTURE arch OF muxing IS
BEGIN
  PROCESS (A, B, Sel) BEGIN
    IF Sel = '1' THEN
      Y <= A;
    ELSE
      Y <= B;
    END IF;
  END PROCESS; END arch;

```

  

## IF statement for memory elements

- ◆ if not all states of an IF statement are defined, a memory element is inserted

```

ENTITY latch IS
  PORT (A: IN  std_logic_vector(3 downto 0);
        write: IN std_logic;
        Y: OUT std_logic_vector(3 downto 0));
END latch;

ARCHITECTURE arch OF latch IS
BEGIN
  PROCESS (A, write) BEGIN
    IF write = '1' THEN
      Y <= A;
    END IF;
  END PROCESS;
END arch;



```



© Copyright 1997 by V. Salapura & M. Gschwind
 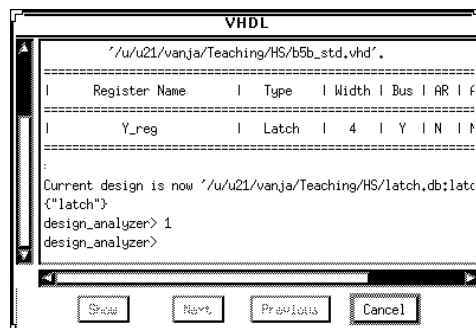
## Latch

- ◆ important: all values have to be defined to avoid memory elements (latches) in combinational logic



© Copyright 1997 by V. Salapura & M. Gschwind

## Flip-flop

### ◆ controlled with clock edge

```



ENTITY flip IS
PORT(A: IN std_logic_vector(3 downto 0);
      clock: IN std_logic;
      Y: OUT std_logic_vector(3 downto 0));
END flip;

```

```

ARCHITECTURE arch OF flip IS
BEGIN
PROCESS (A, clock) BEGIN
  IF clock = '1' AND clock'EVENT THEN
    Y <= A;
  END IF;
END PROCESS; END arch;

```

 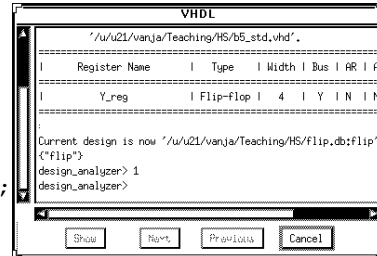

© Copyright 1997 by V. Salapura & M. Gschwind


## IF statements for tri-state buffers

### ◆ all values defined, "Z" used for "others/ELSE"

```

ARCHITECTURE arch OF tri IS
BEGIN
PROCESS (A, write)
BEGIN
  IF write = '1' THEN
    Y <= A;
  ELSE
    Y <= "ZZZZ";
  END IF;
END PROCESS;
END arch;

```

 

© Copyright 1997 by V. Salapura & M. Gschwind

## CASE statement and don't care

- ◆ CASE statements are mapped to multiplexors
- ◆ don't care for better optimization
  - "X" in `std_logic` for synthesis

ARCHITECTURE arch OF casing IS

BEGIN

PROCESS (A, B, C, D, Sel)

BEGIN

CASE Sel IS

WHEN 0 => Y <= A;

WHEN 1 => Y <= B;


WHEN 2 => Y <= C;

WHEN 3 => Y <= D;

WHEN Others => Y <= "XXXX";

END CASE;

END PROCESS; END arch;

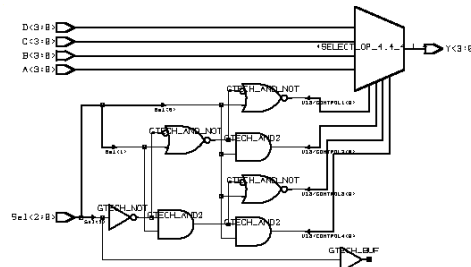

© Copyright 1997 by V. Salapura & M. Gschwind

## Example design - MACC

```

use IEEE.std_logic_1164.all;
use IEEE.std_logic_signed.all;
ENTITY macc IS
  PORT (input1, input2: IN std_logic_vector(3 downto 0);
        reset, clock: IN std_logic;
        out_reg: OUT std_logic_vector(3 downto 0));
END macc;
ARCHITECTURE demo_arch OF macc IS
  SIGNAL new_val, reg: std_logic_vector(3 downto 0);
BEGIN
  Regist: PROCESS(clock, reset) BEGIN
    IF reset = '1' THEN
      reg <= "0000";
    ELSIF clock'EVENT and clock = '1' THEN
      reg <= new_val;
    END IF; END PROCESS;
  Combin: PROCESS(input1, input2, reg)
    VARIABLE new_val1: std_logic_vector(7 downto 0); BEGIN
    new_val1 := input1 * input2;
    new_val <= reg + new_val1(7 downto 4);
  END PROCESS;
  out_reg <= reg; END demo_arch;

```



© Copyright 1997 by V. Salapura & M. Gschwind

## Example design - MACC



### ◆ read the VHDL description

file ⇒ read ⇒ macc.vhd ⇒ OK

```

VHDL
design_analyzer> Loading vhd file /u/u21/vanja/Teaching/HS/macc_std.vf
/u/u21/vanja/Teaching/HS/macc_std.vhd:
Inferred memory devices in process 'Regist'
in routine macc line 24 in file
'/u/u21/vanja/Teaching/HS/macc_std.vhd'.
-----
| Register Name | Type | Width | Bus | AR | RS | SR | SS |
-----
| reg_reg       | Flip-Flop | 4 | Y | Y | IN | IN | IN |
-----
  
```

Show Next Previous Cancel

 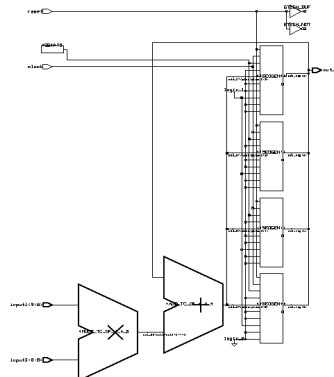


© Copyright 1997 by V. Salapura & M. Gschwind

## Example design - MACC

### ◆ design optimization

- tools ⇒ design optimization ⇒ OK

- file ⇒ save as ⇒ DB, VHDL, SXNF

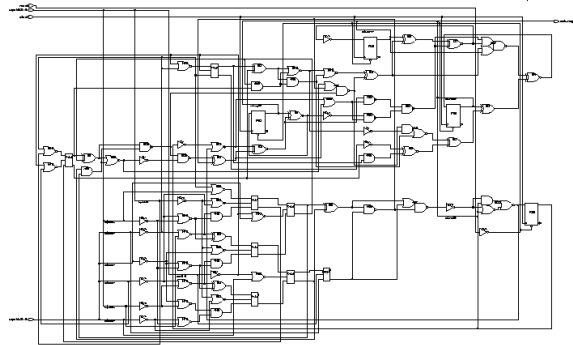

© Copyright 1997 by V. Salapura & M. Gschwind

# Synthesis and Gate Level Simulation with Synopsys

Valentina Salapura  
Michael Gschwind

4-2

## Synopsys design compiler


- ◆ **dominant synthesis tool set in the market**
- ◆ **probably the best synthesis tool available today**
- ◆ **synthesis executed in two steps**
  - **module generator**
    - » VHDL description mapped to modules
    - » modules for operators
    - » technology independent
  - **technology mapping**
    - » modules mapped to gates
    - » technology specific
    - » starting point for the optimization at the gate level

© Copyright 1997 by V. Salapura & M. Gschwind


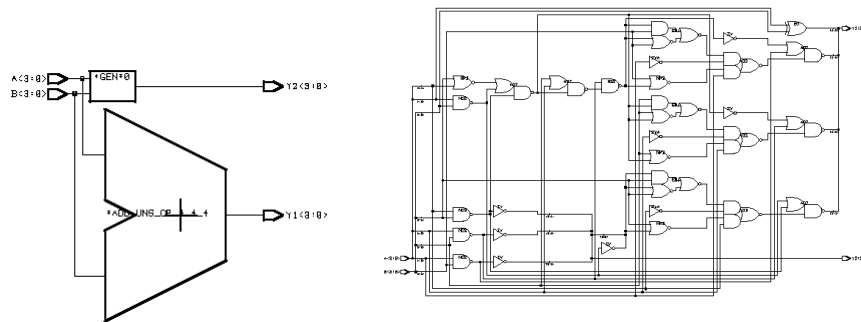
## Two synthesis steps

- ◆ **step 1: simple operators mapped to modules**
- ◆ **step 2: operators mapped to gates and optimization at the gate level**



© Copyright 1997 by V. Salapura & M. Gschwind



## What Synopsys offers

- ◆ **various options for exact specification of**
  - **technology and working environment**
    - » target technology definition
    - » max fan-out, max transition, max capacitance
  - **design optimization**
    - » area and timing optimization
    - » clock specification
    - » various optimization efforts
    - » various optimization methods available (boundary optimization, flatten, Boolean)

© Copyright 1997 by V. Salapura & M. Gschwind



## What can Synopsys do

- read in and use user-defined libraries, packages, etc.
- generate design reports
  - » design complexity (number of gates/technology elements)
  - » design speed
  - » used resources (also as macros from libraries)




## Starting design compiler

- ◆ with "design\_analyzer" for graphical front-end
- ◆ with "dc\_shell" for command line oriented interface
  - graphical front-end translates pull-down menu selections to script commands
    - » can be seen in command window
  - not all commands can be selected using the graphical interface


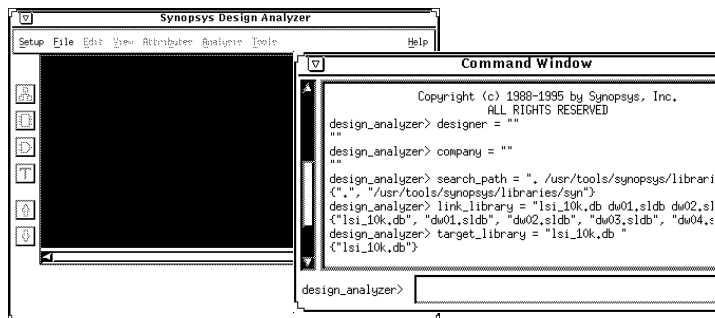
## Selecting commands

- ◆ selecting choices in pull-down menus
- ◆ writing commands in command window
  - open with **setup** ⇒ **command window**
- ◆ directly in **dc\_shell**



© Copyright 1997 by V. Salapura & M. Gschwind



## Working in batch mode

- ◆ using scripts
- ◆ scripts for synthesis control
  - advantageous for complex designs
    - » synthesis and optimization executed unattended over night or longer time
  - also useful for less complex designs
- ◆ each menu selection can be substituted with a script command
- ◆ for advanced usage
  - wider command selection
  - reproducible ⇒ script documents selected synthesis and optimization
  - reduced setup work for repeated synthesis

© Copyright 1997 by V. Salapura & M. Gschwind



## Script language

- ◆ design compiler controlled using script language
- ◆ various command classes for
  - script control
  - reading and saving designs
  - target technology definition
  - translation of VHDL programs
  - definition of module interfaces
  - optimization control
  - report generation



## Script control

- ◆ menu selection  
`setup ⇒ execute script`
- ◆ include scripts in command window and in script files  
`include script_file_name`
- ◆ in program `dc_shell`  
`dc_shell -f script_file_name`



## Reading and saving designs


- ◆ support for various design formats
  - VHDL, Verilog, DB, XNF, EDIF, PLA ...
- ◆ reading designs with `read`
  - example: `read -f xnf macc.xnf`
- ◆ saving designs with `write`
  - option `-hierarchy` saves all submodules
  - example:
 

```
write -f db -hierarchy -output macc.db
```


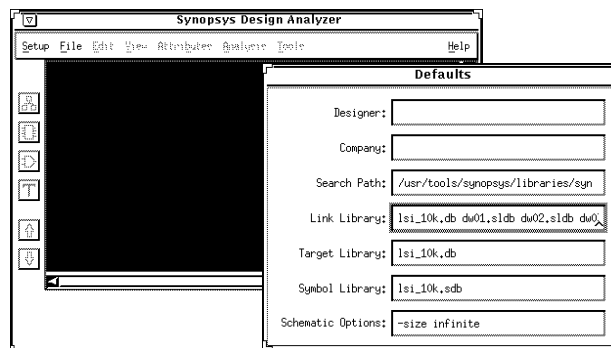
## Technology definition

- ◆ specified in file `.synopsys_dc.setup`
- ◆ menu selection `setup` ⇒ `defaults`



## DesignWare library

- ◆ **module generator**
- ◆ **contains different library elements**
  - implementation of operators +, -, \*, /
  - different modules like RAMs, shift registers, etc.
- ◆ **various implementations for same functionality**
  - different trade-offs, area or speed optimized
- ◆ **appropriate implementation selected automatically in Synopsys as a result of specified design constraints**



© Copyright 1997 by V. Salapura & M. Gschwind

## File .synopsys\_dc.setup

- ◆ **an example of file .synopsys\_dc.setup**

```
search_path = { . /usr/tools/synopsys/libraries/syn }

target_library = lsi_10k.db
link_library = lsi_10k.db
symbol_library = lsi_10k.sdb

/* design ware */

synthetic_library = synthetic_library + { dw01.sldb
dw02.sldb dw03.sldb dw04.sldb dw05.sldb }

link_library = link_library + { dw01.sldb dw02.sldb
dw03.sldb dw04.sldb dw05.sldb }
```




© Copyright 1997 by V. Salapura & M. Gschwind

## Translation of VHDL programs

- ◆ in two steps
  - analyze
    - » translates the design into the working library
  - elaborate
    - » generates design structure from description in the working library
- ◆ menu selections
  - file ⇒ analyze
  - file ⇒ elaborate




## Translation of VHDL programs

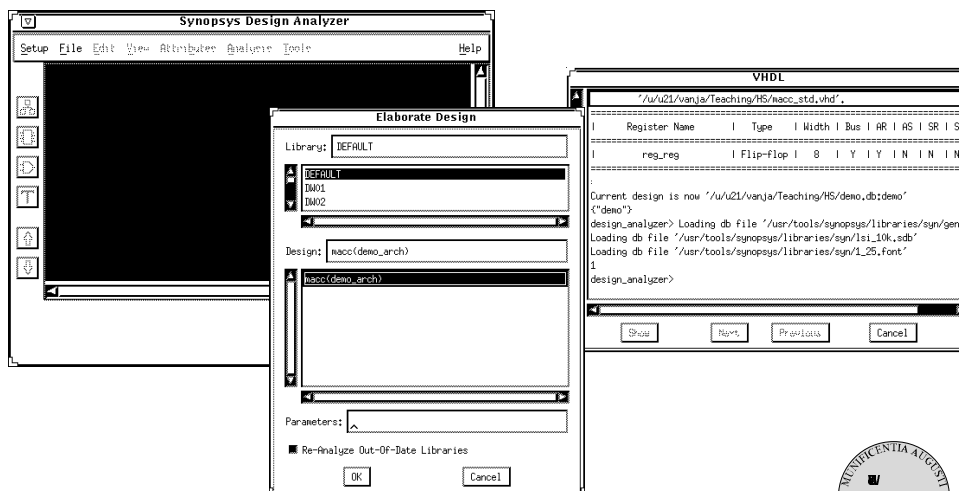
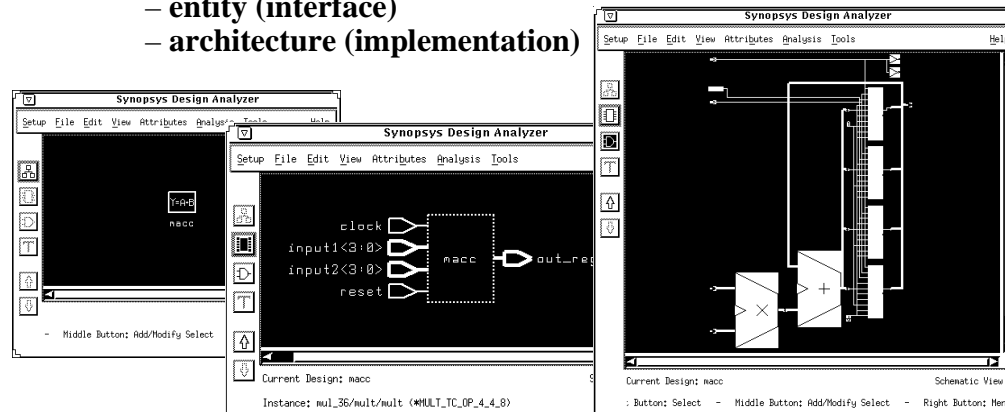
## Different design views

- ◆ design represented at different hierarchical levels
  - module (all modules read)
  - entity (interface)
  - architecture (implementation)



© Copyright 1997 by V. Salapura & M. Gschwind



## Definition of module interfaces

- ◆ ICs require special drivers for external signals ⇒ pads
- ◆ definition of external ports with `set_port_is_pad`
  - typical examples
    - » `set_port_is_pad all_inputs()`
    - » `set_port_is_pad "*"`
- ◆ insertion of pads with `insert_pads`

© Copyright 1997 by V. Salapura & M. Gschwind



## Commands for optimization control

- ◆ design optimization
  - area minimization
  - timing constraints
- ◆ controlling of different optimization methods
  - `set_boundary_optimization`  
`current_design()`
    - » constants on ports propagated to submodules



## Area optimization

- ◆ menu selection attributes ⇒ optimization constraints ⇒ design constraints

The screenshot shows a dialog box titled "Design Constraints". It contains several sections:

- Design Name:** A text field containing the path `me/staff/varja/Teaching/HS/Macc/macc_dbt.macc`.
- Optimization Constraints:**
  - Max Area:** A text field with the value `40`.
  - Max Power:** An empty text field.
- Design Rules:**
  - Max Fanout:** An empty text field.
  - Max Transition:** An empty text field.
- Test Constraints:**
  - Min Fault Coverage:** A text field with the value `95%`.
  - Area Critical:** An unchecked checkbox.
  - Timing Critical:** An unchecked checkbox.

At the bottom of the dialog are two buttons: "Apply" and "Cancel".

- ◆ command `set_max_area 40`



## Signal run time optimization

- ◆ menu selection
  - attributes ⇒ optimization constraints
  - ⇒ timing constraints
- ◆ command `set_max_delay`
  - various options (rise, fall)
  - path specification with start and/or end point
  - `set_max_delay 15 -from port -to port`
- ◆ example
  - `set_max_delay 2 -to out_port`




## Synthesis start

- ◆ optimization constraints have to be set before starting synthesis
- ◆ synthesis started with `compile`
  - example: `compile -map_effort high`
  - additional synthesis control options available


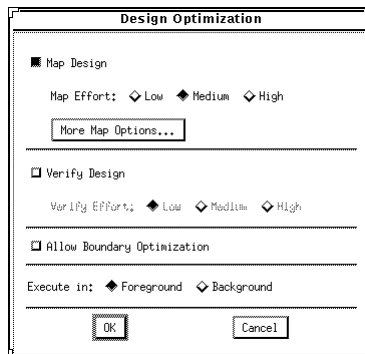
## Starting synthesis

- ◆ starting with  
tools ⇒ design optimization



© Copyright 1997 by V. Salapura & M. Gschwind



## Generating design reports

- ◆ menu selection  
analyze ⇒ report
- ◆ report on resources used  
report\_area
- ◆ signal delay time report  
report\_timing
- ◆ report on FPGA resources  
report\_fpga
- ◆ etc. etc.

© Copyright 1997 by V. Salapura & M. Gschwind



## Area report

### ◆ example: area consumption of design MACC

```

Command Window
1
design_analyzer> report_area
Information: Updating design information... (UID-85)
*****
Report : area
Design : macc
Version : v3,4a
Date : Thu Apr 10 15:20:17 1997
*****
Library(s) Used:
  lsi_10k (File: /usr/tools/synopsys/libraries/sun/lsi_10k.db)
Number of ports:      14
Number of nets:       31
Number of cells:      15
Number of references: 11
Combinational area:  179,000000
Noncombinational area: 36,000000
Net Interconnect area: undefined (No wire load specified)
Total cell area:      215,000000
Total area:           undefined
1
design_analyzer>

```

© Copyright 1997 by V. Salapura & M. Gschwind



## Timing report

```

Command Window
1
design_analyzer> report_timing -path full -delay max -max_paths 1 -worst 1
*****
Report : timing
Design : macc
Version : v3,4a
Date : Thu Apr 10 15:20:19 1997
*****
Operating Conditions:
Wire Loading Model: Hlodt: top
Startpoint: input1<3> (input port)
Endpoint: reg_reg<3> (rising edge-triggered flip-flop clocked by clock)
Path Group: clock
Path Type: max
Point          Iner      Path
-----
clock (input port clock) (rise edge) 0,00      0,00
time 0,00 r
input1<3> (input port) 0,00      0,00 r
mux1_36/mult/mult/B<3> (macc_0M02_mult_4_4_0) 0,00      0,00 r
mux1_36/mult/mult/US<3> (IV6) 0,00      0,00 f
mux1_36/mult/mult/US<3> (IV6) 0,60      1,67 r
mux1_36/mult/mult/US<3> (IV6) 1,07      2,74 r
mux1_36/mult/mult/US<3> (IV6) 0,77      1,89 r
mux1_36/mult/mult/US<3> (IV6) 2,28      6,30 r
mux1_36/mult/mult/US<3> (IV6) 1,19      8,09 f
mux1_36/mult/mult/US<3> (IV6) 0,00      8,09 f
mux1_36/mult/mult/US<3> (IV6) 0,37      9,06 f
mux1_36/mult/mult/US<3> (IV6) 1,32      11,16 f
mux1_36/mult/mult/US<3> (IV6) 0,00      11,16 f
mux1_36/mult/mult/US<3> (IV6) 0,81      11,97 r
mux1_36/mult/mult/US<3> (IV6) 1,14      13,45 f
mux1_36/mult/mult/US<3> (IV6) 1,13      15,66 f
mux1_36/mult/mult/US<3> (IV6) 0,00      15,66 f
reg_reg<3>/D (FI2) 20,00      20,00
data arrival time 0,00      20,00
clock clock (rise edge) 0,00      20,00
clock network delay (ideal) reg_reg<3>/CP (FI2) 0,00      20,00 r
library setup time data required time -0,85      19,15
data arrival time 19,15      19,15
slack (NET) -15,66      3,49
1
design_analyzer>

```

© Copyright 1997 by V. Salapura & M. Gschwind



## Selecting current design

- ◆ all commands executed only on current design
- ◆ current design selection
  - in `design_analyzer`  
clicking on the module
  - in `dc_shell`  
`current_design module_name`



## Other useful commands

- ◆ `ungroup` and `group`
  - for creating and removing hierarchical levels
    - » e.g., to enable optimization over various subdesigns
  - example  
`ungroup -all`
- ◆ `dont_touch`
  - selected module is not further optimized
- ◆ `characterize`
  - transfers design constraints from higher hierarchical level to submodules



## Example of script file

```

read -f vhdl test_add.vhd
current_design add8_impl1
include handle_design_script
report_area > add8_area.out
report_timing -path full -delay max
    -max_paths 1 nworst 1 > add8_time.out
write -f db -hierarchy -o add4_impl1.db
◆ file handle_design_script:
set_port_is_pad
ungroup current_design()
set_boundary_optimization current_design()
compile -ungroup_all -map_effort medium

```

© Copyright 1997 by V. Salapura & M. Gschwind



## Gate level simulation

- ◆ to simulate at the gate level
  - generate a simulation library from the synthesis library
  - analyze the simulation library
  - reference the simulation library in gate-level description
  - generate an SDF file from a design
  - start the simulation using the SDF file

© Copyright 1997 by V. Salapura & M. Gschwind



## Standard delay format (SDF)

- ◆ SDF is a standard delay format
  - portable description of design delays
  - supported by many EDA tools
- ◆ contains timing information of a synthesized design
- ◆ for back-annotating design timing with gate-level simulation



## Generating simulation library

- ◆ simulation library is generated from the synthesis library file *lib\_name.db*
  - `liban -arch model lib_name.db`
  - option `-arch` specifies one of five timing models
    - » `ftbm` – accurate timing model, slowest simulation
    - » `udsm` – all cells with 1ns delay, fastest simulation
    - » `ftsm` – each cell with accurate timing, less accurate than `ftbm`, slower simulation than `udsm`
    - » `ftgs` – as accurate as `ftbm`, fast simulation (optimized for Synopsys)
    - » `vital` – vital model
- ◆ results of compilation are files `lib_name_components.vhd` and `lib_name_FTSM.vhd.E`



## Analyzing simulation library

- ◆ simulation library has to be analyzed

```
vhdlan -w lib_name
      lib_name_FTSM.vhd.E
      lib_name_components.vhd
```
- ◆ timing model library files are compiled and stored in the simulation library *lib\_name*



## Using the simulation library

- ◆ simulation libraries are similar to other libraries
- ◆ simulation library has to be
  - specified in the setup file
  - referenced in the VHDL description



## Specifying simulation library

- ◆ simulation library has to be specified in the setup file `.synopsys_vss.setup`
- ◆ for simulation library generated from LSI 10k synthesis library example
  - insert in the file `.synopsys_vss.setup`

```
LSI_10K: $SYNOPSIS/libraries/sim/lsi_10k
```



## Referencing simulation library

- ◆ simulation library has to be referenced in the VHDL file to be simulated
  - for the LSI 10k example
    - » insert in the VHDL gate level file

```
library lsi_10k;
use lsi_10k.components.all
```
- ◆ this can be automated by putting the following command in the setup file `.synopsys_dc.setup`

```
vhdlout_use_packages =
  {"LSI_10K.COMPONENTS"};
```



## Generating an SDF file from a design

- ◆ SDF file contains timing information of a synthesized design
  - required for gate level simulation
- ◆ generation in command window
  - select file format for VHDL simulation

```
change_names -rules vhdl -hierarchy
```

  - generate SDF file

```
write_timing -format sdf -output
  sdf_file_name
```



## Starting the gate level simulation

- ◆ gate level simulation uses the timing information from an SDF file
- ◆ gate level simulation has to be started in command mode
 

```
vhdlsim -sdf_top /tb/uut
  -sdf sdf_file_name cfg_tb_name
```

  - option `-sdf_top` specifies the design described by SDF file is (UUT in the above example)
  - the last argument (`cfg_tb_name`) specifies the test bench configuration



## Simulation in command mode

- ◆ **command mode simulator vhdlsim uses the same commands as the window mode vhdldb**
  - **trace**
    - » signal selection for waveforms
  - **cd**
    - » moving through the program hierarchy
  - **step, next**
    - » execute simulation in steps
  - **run *time\_expression***
    - » simulation start
  - **include**
    - » usage of scripts




## Simulation example: MACC gate-level description

```

library IEEE;
library LSI_10K;
use IEEE.std_logic_1164.all;
use LSI_10K.COMPONENTS.all;
entity macc is
    port(input1,input2: in std_logic_vector (3 downto 0);
         reset,clock: in std_logic;
         out_reg : out std_logic_vector (7 downto 0));
end macc;
architecture SYN_demo_arch of macc is
    component IVA
        port(A: in std_logic; Z : out std_logic);
    end component;
    component FD2
        port(D,CP,CD: in std_logic; Q,QN: out std_logic);
    end component;
    ...

```

referencing the simulation library

 

## Simulation example: MACC SDF file


```

DELAYFILE
(SDFVERSION "OVI 1.0")
(DESIGN "macc")
(DATE "Tue May 13 15:37:44
1997")
(VENDOR "lsi_10k")
(PROGRAM "Synopsys Design
Compiler cmos")
(VERSION "v3.4a")
(DIVIDER /)
(VOLTAGE 5.00:5.00:5.00)
(PROCESS)
(TEMPERATURE
25.00:25.00:25.00)
(TIMESCALE 1ns)

(CELL
(CELLTYPE "FA1A")
(INSTANCE add_37_plus_plus/U1_5)
(DELAY
(ABSOLUTE
(IOPATH A CO (2.182:2.182:2.182)
(2.274:2.274:2.274))
(IOPATH B CO (2.182:2.182:2.182)
(2.274:2.274:2.274))
(IOPATH CI CO (1.082:1.082:1.082)
(1.174:1.174:1.174))
(IOPATH A S (2.136:2.136:2.136)
(1.925:1.925:1.925))
(IOPATH B S (2.136:2.136:2.136)
(1.925:1.925:1.925))
(IOPATH CI S (1.036:1.036:1.036)
(0.825:0.825:0.825)) ))

```

 © Copyright 1997 by V. Salapura & M. Gschwind



## Simulation example: starting the simulation

- ◆ simulation started with

```

vhdlsim -sdf_top /tb/uut
-sdf macc.timing cfg_tb_macc

```
- ◆ simulation performed as usual

```


cd tb
trace clock res in1 in2 result
run 400

```

© Copyright 1997 by V. Salapura & M. Gschwind



# Simulation example: waveforms

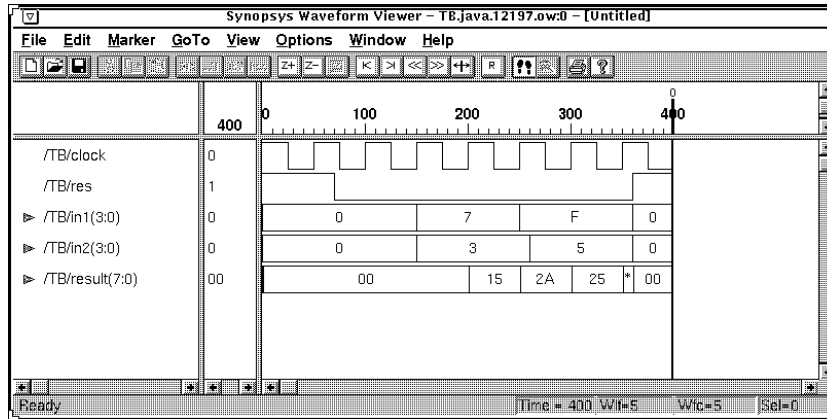

© Copyright 1997 by V. Salapura & M. Gschwind



# Exercise 2

## Synthesis and gate level simulation

Valentina Salapura  
Michael Gschwind

E2-2

### Synthesis and gate level simulation

- ◆ use ALU description from exercise 1 as a starting point
- ◆ modify ALU to use `std_logic_vector` for inputs and output
- ◆ synthesize the ALU for an ASIC target technology
  - e.g., LSI 10k included in Synopsys standard distribution

© Copyright 1997 by V. Salapura & M. Gschwind



## Complete the following tasks

- ◆ **synthesize and optimize the ALU**
  - optimized for area
  - optimized for timing
- ◆ **compare results generated by area and timing optimization**
- ◆ **explain why `after` clause is ignored**
- ◆ **simulate the synthesis results using test bench from exercise 1**
- ◆ **explain why only a subset of VHDL can be synthesized**



# Modeling Sequential Logic and Finite State Machines

Valentina Salapura  
Michael Gschwind

5-2

## Building complex VHDL models

- ◆ **VHDL supports modeling at different abstraction levels**
  - language constructs for each abstraction level
  - **behavioral level**
    - » functions, procedure calls, processes
  - **register transfer level (RTL)**
    - » concurrent statements and formulae
  - **structural level (VHDL netlist)**
    - » components, component instantiation, component interconnections



## Hybrid descriptions

- ◆ language constructs for different abstraction levels can be mixed in a single description
  - using constructs of all abstraction levels in single architecture
    - » process for algorithm description
    - » RTL formulae
    - » component instantiation
  - useful for simulation and synthesis
    - » re-use of existing modules in description of new modules through component instantiation
    - » mixing of descriptions with different amount of detail



## Component declaration and instantiation

- ◆ component declared in the declaration part of an architecture body
- ◆ syntax
 

```
component identifier is
    generic (generic_constants_list);
    port (port_list);
end component;
```
- ◆ component instantiated in the statements part of an architecture body
- ◆ syntax
 

```
label: name generic map (generic_list);
    port map (port_list);
```



## Hybrid design example: MACC

```

ARCHITECTURE demo_arch OF macc IS
  COMPONENT multy
    PORT(in1, in2: IN std_logic_vector(3 downto 0);
         res: OUT std_logic_vector(3 downto 0));
  SIGNAL new_val, reg, res: std_logic_vector(3 downto 0);
BEGIN
  Reg: PROCESS(clock, reset) BEGIN
    IF reset = '1' THEN
      reg <= "0000";
    ELSIF clock'EVENT AND clock = '1' THEN
      reg <= new_val;
    END IF;
  END PROCESS;


  Multiply: multy port map(input1, input2, res);
  new_val <= reg + res;
  out_reg <= reg;
END demo_arch;

```

© Copyright 1997 by V. Salapura & M. Gschwind



## Hybrid design example: MACC schematic

 

© Copyright 1997 by V. Salapura & M. Gschwind



## Synthesis of sequential logic


- ◆ to synthesize sequential logic need to define
  - clock(s) – requires special treatment
    - » stronger drivers
    - » uniform distribution
  - memory element type
    - » selection of flip flops and latch types to be generated by logic synthesis
    - » type of memory element (whether flip flops or latches are used) depends on VHDL description style



© Copyright 1997 by V. Salapura & M. Gschwind
 
## Setting the clock

- ◆ menu selection attributes ⇒ clocks ⇒ specify
  - for selected port of a module
  - set clock period and edges



© Copyright 1997 by V. Salapura & M. Gschwind

## Clock specification

- ◆ in dc\_shell and in command window

```
create_clock -name "clock" -period 20
-waveform {0 10} find(port,"clock")
```

- ◆ explanation

```
-name "clock"
  » specify clock name
-period 20
  » period of the clock
-waveform {"0" "10"}
  » rise and fall times for one period
-find(port,"clock")
  » clock is specified for this port
```



## Selection of memory elements type

- ◆ selection of particular flip flops or latches styles

- optional

- ◆ for exact specification of memory elements

```
set_register_type -flip_flop "FD1S"
```

- » simple edge-triggered D flip flop

```
set_register_type -latch -exact "LD1P"
```

- » positive edge active D latch

- ◆ menu selection

```
attributes ⇒ optimization directives ⇒ design
attributes
```



## Description of memory elements

- ◆ memory elements generated for signals which are not defined for all possible conditions in conditional assignments
- ◆ the type of memory element generated inferred implicitly from the VHDL description
  - flip-flop
    - » edge-triggered
  - latch
    - » level sensitive



© Copyright 1997 by V. Salapura & M. Gschwind



## Flip-flop register

```

ENTITY ff_bank IS
PORT (A: IN  std_logic_vector
      (3 downto 0);
      clock: IN std_logic;
      Y: OUT std_logic_vector
      (3 downto 0));
END ff_bank;

ARCHITECTURE arch OF ff_bank IS
BEGIN
  PROCESS (A, clock) BEGIN
    IF clock = '1' AND clock'EVENT THEN
      Y <= A;
    END IF;
  END PROCESS;
END arch;

```

 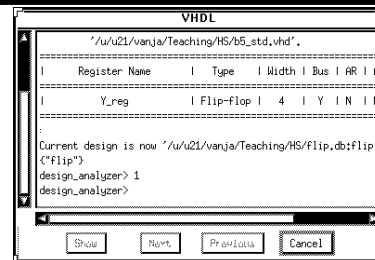

© Copyright 1997 by V. Salapura & M. Gschwind

## Latch register

```



ENTITY latch_bank IS
  PORT(A: IN  std_logic_vector
        (3 downto 0);
        write: IN std_logic;
        Y: OUT std_logic_vector
        (3 downto 0));
END latch_bank;

```

```

ARCHITECTURE arch OF latch_bank IS
BEGIN
  PROCESS (A, write) BEGIN
    IF write = '1' THEN
      Y <= A;
    END IF;
  END PROCESS;
END arch;

```

 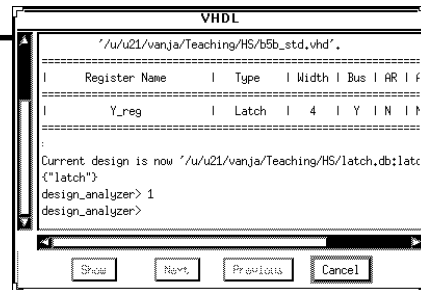

© Copyright 1997 by V. Salapura & M. Gschwind

## Combinational and sequential logic

- ◆ most designs contain *both* combinational and sequential logic

```

LIBRARY IEEE, work;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_signed.all;
use work.all;

ENTITY abff IS
  PORT(A,B: IN std_logic_vector
        (3 downto 0);
        clock,reset: IN std_logic;
        Y: OUT std_logic_vector
        (3 downto 0));
END abff;

```

```


ARCHITECTURE arch OF abff IS
BEGIN
  PROCESS (clock, reset)
  BEGIN
    IF reset = '1' THEN
      Y <= "0000";
    ELSIF clock'EVENT AND
          clock = '1' THEN
      Y <= A + B;
    END IF;
  END PROCESS;
END arch;

```



© Copyright 1997 by V. Salapura & M. Gschwind

## Synthesized design

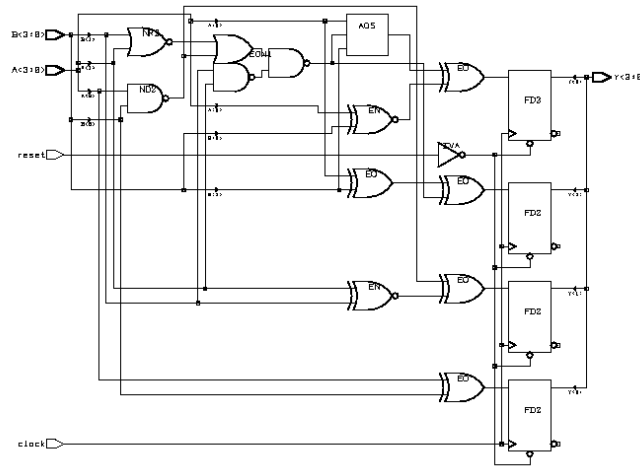

© Copyright 1997 by V. Salapura & M. Gschwind



## Design initialization

- ◆ all registers in a design are set to an initial value
- ◆ registers can be initialized using
  - synchronous reset
    - » executed on the next clock edge
    - » activated by positive or negative clock edge
  - asynchronous reset
    - » executed independently on the clock

© Copyright 1997 by V. Salapura & M. Gschwind




## Synchronous reset

```

PROCESS (clock, reset, A)
BEGIN
  IF clock'EVENT AND clock = '1' THEN
    IF reset = '1' THEN
      Q <= '0';
    ELSE
      Q <= A;
    END IF;
  END IF;
END PROCESS;

```

 

© Copyright 1997 by V. Salapura & M. Gschwind




## Asynchronous reset

```

PROCESS (clock, reset, A)
BEGIN
  IF reset = '1' THEN
    Q <= '0';
  ELSIF clock'EVENT AND
    clock = '1' THEN
    Q <= A;
  END IF;
END PROCESS;

```

 

© Copyright 1997 by V. Salapura & M. Gschwind



## Example sequential logic: counter

- ◆ synchronous 8-bit counter
- ◆ asynchronous reset
- ◆ selection between counting up and down
  - selected with signal `dir`
  - increments if `dir = '1'`
  - decrements if `dir = '0'`



© Copyright 1997 by V. Salapura & M. Gschwind

## VHDL implementation of the counter

```
ENTITY counter IS
  PORT (
    reset : IN  std_logic;
    clock  : IN  std_logic;
    dir    : IN  std_logic;
    count_out: OUT
      std_logic_vector
      (7 downto 0));
END counter;


ARCHITECTURE arch OF counter
  IS
    SIGNAL count:
      std_logic_vector
      (7 downto 0);
  BEGIN
```

```
Count_reg: PROCESS (clock, reset)
  BEGIN
    IF reset = '1' THEN
      count <= "00000000";
    ELSIF clock'EVENT AND
      clock = '1' THEN
      IF dir = '1' THEN
        count <= count + 1;
      ELSE
        count <= count - 1;
      END IF; END IF;
    END PROCESS;
  count_out <= count;
END arch;
```




© Copyright 1997 by V. Salapura & M. Gschwind
 
# Elaboration generates structural representation



 
© Copyright 1997 by V. Salapura & M. Gschwind



# Optimized synthesis result

```

Command Window
=====
Report : resources
Design : counter
Version : v5.4a
Date   : Tue Apr 15 13:41:24 1997
=====
Resource Sharing Report for design counter in file
/u/u21/vanjs/Teaching/HS/counter.vhd
=====
| Resource | Module | Parameters | Resources | Contained Operations |
|-----|-----|-----|-----|-----|
| r72     | IM01_indec | width=8 | | add_25/plus/plus |
|         |          |         | | sub_27/minus/minus |
=====
Implementation Report
=====
| Cell | Module | Implementation | Implementation |
|-----|-----|-----|-----|
| U30  | IM01_indec | rpl | |
=====
No multiplexers to report
design_analyzer>
    
```

 

© Copyright 1997 by V. Salapura & M. Gschwind



## Example sequential logic: serial-to-parallel converter

- ◆ serial-to-parallel converter
- ◆ synchronous 8 bit conversion
- ◆ asynchronous reset
- ◆ accepts serial data stream
- ◆ packs 8 bits in a byte
- ◆ outputs byte



© Copyright 1997 by V. Salapura & M. Gschwind

## Serial/parallel source

```


ENTITY parallel IS
  PORT (
    reset : IN  std_logic;
    clock : IN  std_logic;
    data_i: IN  std_logic;
    data_o: OUT std_logic_vector
              (7 downto 0));
END parallel;

ARCHITECTURE arch OF parallel IS
  SIGNAL reg: std_logic_vector
            (7 downto 0);
  SIGNAL count: std_logic_vector
            (2 downto 0);
BEGIN
  Shift: PROCESS(clock, reset)
  BEGIN
    IF reset = '1' THEN
      reg <= "00000000";
    ELSIF clock'EVENT AND clock= '1' THEN
      reg <= data_i & reg(7 downto 1);
    END IF; PROCESS;

  Counter: PROCESS(clock, reset)
  BEGIN
    IF reset = '1' THEN
      count <= "000";
    ELSIF clock'EVENT AND clock= '1' THEN
      count <= count + 1;
    END IF; END PROCESS;


  data_o <= reg WHEN count = "111"
            ELSE "00000000";
END arch;

```

 

© Copyright 1997 by V. Salapura & M. Gschwind

## Implementation

 

© Copyright 1997 by V. Salapura & M. Gschwind



## Description of finite state machines


- ◆ finite state machines important in hardware design
  - for design of control units
- ◆ finite state machines = FSM
- ◆ two types of FSM
  - Mealy FSM
  - Moore FSM

© Copyright 1997 by V. Salapura & M. Gschwind


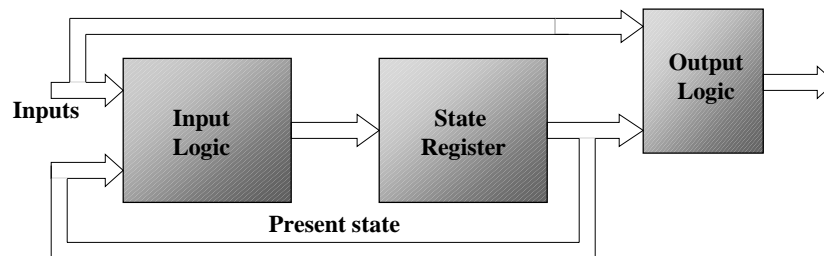
## Mealy finite state machines

- ◆ outputs of the Mealy FSM depend on the current state of the machine and on the current inputs




© Copyright 1997 by V. Salapura & M. Gschwind


 
## Moore finite state machines

- ◆ outputs of the Moore FSM depend only on the current state of the machine



© Copyright 1997 by V. Salapura & M. Gschwind



## VHDL description styles of FSM

- ◆ **FSM description style depends on**
  - **number of state signals**
    - » **one signal for modeling both current and next state of the FSM**
    - » **two signals used for describing current and next state of the FSM**
  - **number of processes in the architecture**
  - **how combinational and sequential logic are allocated to processes**




## Explicit description

```

ENTITY fsm IS
PORT (
  reset, clock: IN std_logic;
  F, G : OUT  std_logic);
END fsm;
ARCHITECTURE expl OF fsm IS
  TYPE state_type IS
    (idle, start, stop, clear);
  SIGNAL state: state_type;
BEGIN
  PROCESS(clock, reset, state)
  BEGIN
    IF clock'EVENT AND clock= '1' THEN
      IF reset = '1' THEN
        state <= idle;
        F <= '0'; G <= '0';
      ELSE
        CASE state IS
        WHEN idle => state <= start;
          G <= '0';
        WHEN start => state <= stop;
        WHEN stop => state <= clear;
          F <= '1';
        WHEN clear => state <= idle;
          F <= '0'; G <= '1';
        END CASE;END IF;END IF;END PROCESS;
    END expl;
  
```



## Resulting design

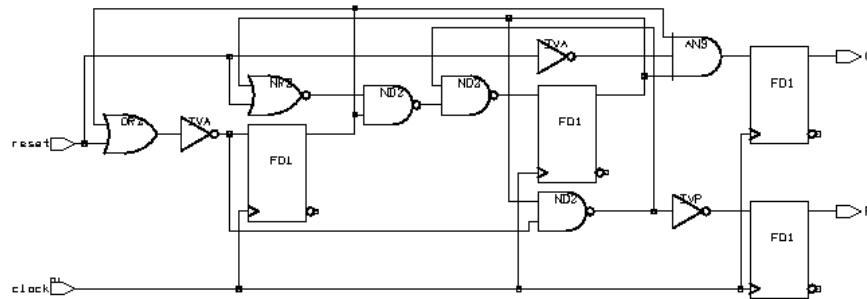

© Copyright 1997 by V. Salapura & M. Gschwind



## Separated generation of outputs

```

ARCHITECTURE separate OF fsm IS
  TYPE state_type IS
    (idle, start, stop, clear);
  SIGNAL state: state_type;
BEGIN
Output: PROCESS(state)
  BEGIN
    F <= '0';
    G <= '0';
    IF state = clear THEN
      F <= '1';
    END IF;
    IF state = idle THEN
      G <= '1';
    END IF;
  END PROCESS;

```

```


Transition: PROCESS(clock)
  BEGIN
    IF clock'EVENT AND clock = '1'
      THEN
        IF reset='1' OR state=clear THEN
          state <= idle;
        ELSIF state = idle THEN
          state <= start;
        ELSIF state = start THEN
          state <= stop;
        ELSE
          state <= clear;
        END IF; END IF;
    END PROCESS;
  END separate;

```

© Copyright 1997 by V. Salapura & M. Gschwind



## Resulting design

 

© Copyright 1997 by V. Salapura & M. Gschwind



## Separated sequential and combinational logic

```

ARCHITECTURE reg OF fsm IS
  TYPE state_type IS
    (idle, start, stop, clear);
  SIGNAL state, next_state:
    state_type;
BEGIN
  State_reg: PROCESS(clock)
  BEGIN
    IF clock'EVENT AND clock = '1'
    THEN
      IF reset = '1' THEN
        state <= idle;
      ELSE
        state <= next_state;
      END IF; END IF;
    END PROCESS;

```

```

Combination: PROCESS(state)
BEGIN
  F <= '0'; G <= '0';
  IF state = clear THEN
    next_state <= idle;
    F <= '1';
  ELSIF state = idle THEN
    next_state <= start;
    G <= '1';
  ELSIF state = start THEN
    next_state <= stop;
  ELSE
    next_state <= clear;
  END IF; END PROCESS;
END reg;

```

© Copyright 1997 by V. Salapura & M. Gschwind



## Separated in three processes

```

ARCHITECTURE three OF fsm IS
  TYPE state_type IS
    (idle, start, stop, clear);
  SIGNAL state, next_state:
    state_type;
BEGIN
  State_reg: PROCESS (clock)
  BEGIN
    IF clock'EVENT AND
      clock = '1' THEN
      IF reset = '1' THEN
        state <= idle;
      ELSE
        state <= next_state;
      END IF; END IF;
    END PROCESS;

  Comb_Output: PROCESS (state) BEGIN
  CASE state IS
    WHEN clear => next_state <= idle;
    WHEN idle => next_state <= start;
    WHEN start => next_state <= stop;
    WHEN others => next_state <= clear;
  END CASE;
  END PROCESS;

  Output: PROCESS (state) BEGIN
    F <= '0'; G <= '0';
    IF state = clear THEN
      F <= '1';
    ELSIF state = idle THEN
      G <= '1';
    END IF;
  END PROCESS;
END three;

```

© Copyright 1997 by V. Salapura & M. Gschwind



## Comparison of description styles

description style	# of state signals	# of processes	# FFs	# of gates	
explicit	1	1	4	39	wrong functionality!!!
separated outputs	1	2	2	24	
separated seq. und comb.	2	2	2	24	
3 processes	2	3	2	24	

© Copyright 1997 by V. Salapura & M. Gschwind



# Resource Sharing

Valentina Salapura  
Michael Gschwind

6-2

## Resource sharing

- ◆ **single functional unit used several times from different design parts**
  - for example, for two “+” in source code sometimes can be used the same adder
- ◆ **resource sharing (RS) tries to allocate different operators to same functional unit**
- ◆ **the quality of resource sharing depends on the synthesis tool**



## How resource sharing works

- ◆ in most synthesis tools resource sharing depends on results of static analysis
  - resource sharing generated only for statically disjoint operations
    - » for example, in different branches of IF and CASE statements
- ◆ resource sharing introduces multiplexors to multiplex various inputs to the shared unit
  - multiplexor introduces additional delay



## Resource sharing example: accumulator

- ◆ implement 8-bit accumulator
- ◆ synchronous reset
- ◆ adds or subtracts input
  - operations + or - selected with signal `ctl`
  - add if `ctl = '1'`
  - subtract if `ctl = '0'`
- ◆ both operations should use the same add/subtract unit



## RS example: VHDL description

```

ENTITY accu IS
  PORT (
    reset   : IN   std_logic;
    clock   : IN   std_logic;
    ctl     : IN   std_logic;
    data_in : IN   std_logic_vector
              (3 downto 0);
    data_out: OUT  std_logic_vector
              (7 downto 0));
END accu;

ARCHITECTURE arch OF accu IS
  SIGNAL accu:
    std_logic_vector
      (7 downto 0);
BEGIN
  Accumulator:PROCESS (clock,reset)
  BEGIN
    IF reset = '1' THEN
      accu <= "00000000";
    ELSIF clock'EVENT AND
      clock = '1' THEN
      IF ctl = '1' THEN
        accu <= accu + data_in;
      ELSE
        accu <= accu - data_in;
      END IF; END IF;
    END PROCESS;
  data_out <= accu;
END arch;

```

© Copyright 1997 by V. Salapura & M. Gschwind




## RS example: elaboration result

◆ schematic generated from VHDL description during elaboration

– no resource sharing

» addition and subtraction mapped to two units

two separate units for add and subtract

 

© Copyright 1997 by V. Salapura & M. Gschwind




## RS example: optimized design

- ◆ RS introduced in optimization
  - resource report lists shared units and operations mapped to them

```

Command Window
Report : resources
Design : acou
Version: 1997_01
Date   : Tue Sep  9 17:20:53 1997
*****
Resource Sharing Report for design acou in file
/home/staff/vanja/Teaching/RS/MSL/acou.vhd
-----
| Resource | Module | Parameters | Contained | Contained Operations |
|-----|-----|-----|-----|-----|
| r19      | DM01_addsub | width=8 | | add_26/plus/plus |
|         |          |          | | sub_26/minus/minus |
|-----|-----|-----|-----|-----|
Implementation Report
-----
| Cell      | Module | Current | Set | Implementation | Implementation |
|-----|-----|-----|-----|-----|-----|
| No multiplexors to report
| design_analyzer>
design_analyzer>
  
```

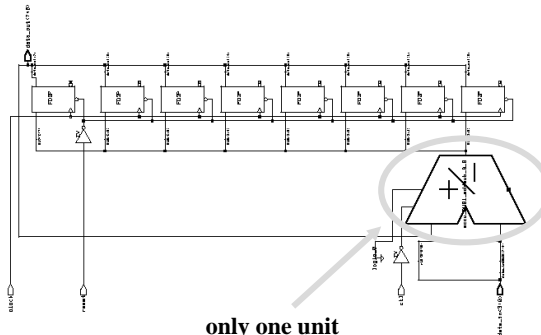

only one unit  
for add and subtract  
operations



© Copyright 1997 by V. Salapura & M. Gschwind

## Resource sharing in Synopsys


- ◆ options
  - no RS
  - automatic RS
  - user controlled RS
- ◆ automatic RS used by default
  - only if design timing allows introduction of additional delay for multiplexor
  - RS problem for time constrained designs



© Copyright 1997 by V. Salapura & M. Gschwind
 
## Time constrained designs

- ◆ **automatic RS can be problem for timing critical designs**
  - RS introduces multiplexor for different resource inputs  $\Rightarrow$  design slowed down
  - even a minimal timing violation eliminates RS
  - possible result  $\Rightarrow$  resource explosion
  - solution: user controlled RS



## User controlled resource sharing

- ◆ **synthesis tool sometimes generates no RS**
  - does not recognize that a functional unit can be shared
- ◆ **user can still control synthesis tool to introduce RS**
  - introduced by describing it in VHDL programs
- ◆ **user defines resources which are to be shared**
  - using VHDL construct `attribute`
  - VHDL description has to be modified



## Automatic RS example: VHDL source

```
LIBRARY IEEE, work;
use IEEE.std_logic_1164.ALL;
use IEEE.std_logic_signed.ALL;
use work.ALL;
```

```
ENTITY share IS
PORT (
  A,B,C: IN  std_logic_vector
        (7 downto 0);

  cnt1: IN  std_logic;
  cnt2: IN  std_logic;
  Y:      OUT std_logic_vector
        (7 downto 0));
END share;
```

```
ARCHITECTURE arch OF share IS
BEGIN
  PROCESS (A, B, C, cnt1, cnt2)
  BEGIN
    IF cnt1 = '1' THEN
      Y <= A + B;
    ELSIF cnt2 = '1' THEN
      Y <= A + C;
    ELSE
      Y <= "00000000";
    END IF;
  END PROCESS;
END arch;
```


share one adder  
for these operations





© Copyright 1997 by V. Salapura & M. Gschwind

## Automatic RS example: synthesis results

### elaboration result

 

### RS introduced during optimization

 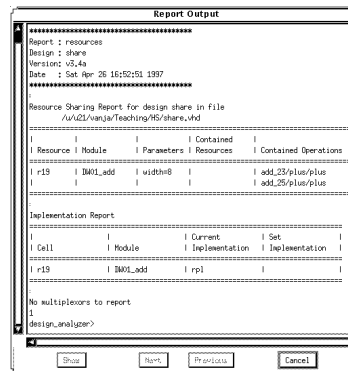

© Copyright 1997 by V. Salapura & M. Gschwind

## No RS example: VHDL source

```

LIBRARY IEEE, work;
use IEEE.std_logic_1164.ALL;
use IEEE.std_logic_signed.ALL;
use work.ALL;

ENTITY no_share IS
  PORT (
    A,B:  IN  std_logic_vector
           (7 downto 0);
    cnt1: IN  std_logic;
    cnt2: IN  std_logic;
    Y:    OUT std_logic_vector
           (7 downto 0));
END no_share;

```

```

ARCHITECTURE arch OF no_share IS
BEGIN
  PROCESS (A, B, cnt1, cnt2)
  BEGIN
    IF cnt1 = '1' THEN
      Y <= A + B;
    ELSIF cnt2 = '1' THEN
      Y <= A - 1;
    ELSE
      Y <= "00000000";
    END IF;
  END PROCESS;
END arch; these two operations
                can share one add/sub unit


```

© Copyright 1997 by V. Salapura & M. Gschwind




## No RS example: synthesis results

### elaboration result

 


two separate units

### no RS introduced in optimization

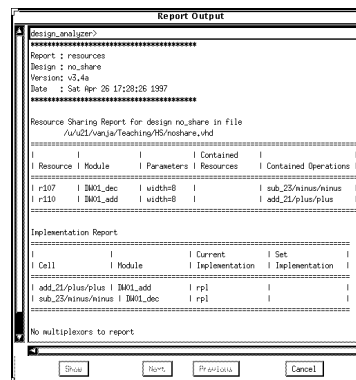

### still two units

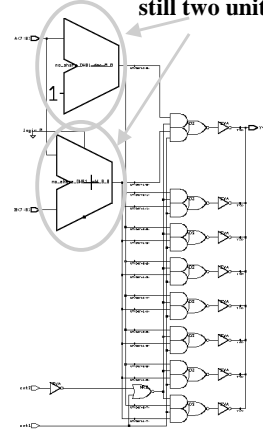

© Copyright 1997 by V. Salapura & M. Gschwind



## User controlled RS example: VHDL source

```

LIBRARY IEEE, work;
use IEEE.std_logic_1164.ALL;
use IEEE.std_logic_signed.ALL;
use work.ALL;

ENTITY uc_share IS
  PORT (
    A,B: IN ...;
    cnt1,cnt2: IN ...;
    Y: OUT ...;
  )
END uc_share;

ARCHITECTURE arch OF uc_share IS
BEGIN
  PROCESS(A, B, cnt1, cnt2)
  SUBTYPE resource IS integer;
  ATTRIBUTE ops: string;
  CONSTANT adder: resource := 0;
  ATTRIBUTE ops OF adder:
    constant IS "ADD DEC";
  BEGIN
    IF cnt1 = '1' THEN
      Y <= A + B;
      -- pragma label ADD
    ELSIF cnt2 = '1' THEN
      Y <= A - 1;
      -- pragma label DEC
    ELSE
      Y <= "00000000";
    END IF; END PROCESS;
  END arch;


```

changes in VHDL code for user controlled RS


© Copyright 1997 by V. Salapura & M. Gschwind


 
## User controlled RS example: synthesis results



only one add/sub unit

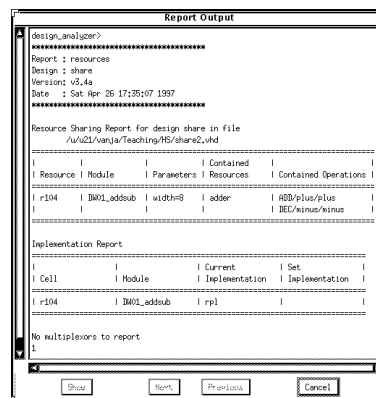

© Copyright 1997 by V. Salapura & M. Gschwind



## What resources can be shared

- ◆ not all resources can be shared
- ◆ RS possible for units with similar functionality
- ◆ typically
  - ‘+’ and ‘+’
  - ‘+’ and ‘-’
  - ‘.’ and ‘.’
  - ‘>’ and ‘>’
  - ‘>’ and ‘<’
  - ‘<’ and ‘<=’
  - ‘>’ and ‘<=’
- ◆ exact set depends on synthesis tool



## Resource implementation

- ◆ Synopsys supports several implementations for the same functional unit
  - i.e., several different adder implementations available in DesignWare library
    - » `cla` – carry look-ahead synthesis model
    - » `rp1` – ripple carry synthesis model
    - » `clf` – fast carry look-ahead synthesis model
    - » `sim` – simulation model
  - additional implementations available
    - » from ASIC vendor optimized for target process
    - » from IP vendors



## Selecting resource implementation

- ◆ **resource implementation can be selected**
  - **indirectly – by setting constraints**
    - » e.g. for fast design, `c1a` model is chosen
    - » e.g. for small design, `rp1` model is included
  - **directly**
    - » **modifying the VHDL description to select the desired implementation**
    - » **forbidding the optimizer to use slow implementations, e.g. using command to forbid ripple carry model**  
`set_dont_use standard.sldb/*/rp1`



# Exercise 3


## Design reuse and integration

Valentina Salapura  
Michael Gschwind

E3-2
 
## Design reuse and integration

- ◆ design a digital thermometer
- ◆ thermometer can display temperature in °C or °F
- ◆ advantageous over analog thermometer
  - selection °F/°C with switch
    - »  $C/\bar{F} = 0$ , output in °F, convert input from °C to output in °F
    - »  $C/\bar{F} = 1$ , output in °C, no conversion required




© Copyright 1997 by V. Salapura & M. Gschwind


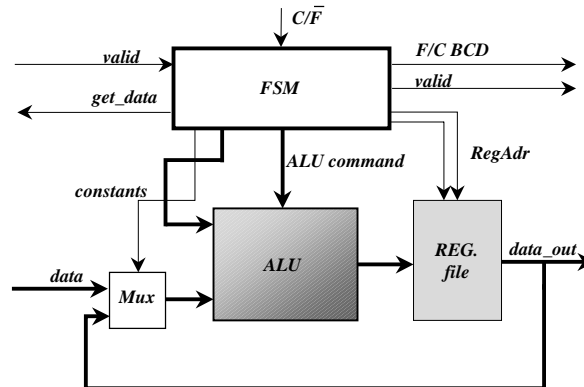
## Design overview

- ◆ conversion formula

$$^{\circ}\text{F} = ^{\circ}\text{C} * 2 + 32$$



© Copyright 1997 by V. Salapura & M. Gschwind



## Explanation of functional units

- ◆ design an FSM for controlling design
- ◆ design reuse – use existing designs for
  - ALU
  - register file
- ◆ use ALU from exercise 2
  - functionality must not be changed
- ◆ use register file from DesignWare library
  - use component DW03\_ram2\_s\_d
  - data sheet for component
    - » in Synopsys online documentation

© Copyright 1997 by V. Salapura & M. Gschwind



## Control flow of the thermometer

- ◆ start A/D converters using signal `get_data`
- ◆ wait for results from the A/D converter
  - signal `valid` – data available
  - signal `data` – temperature in °C
- ◆ convert the temperature from °C into °F
  - if required, i.e., signal  $C/\overline{F} = 0$
  - use register file for storing intermediate results
- ◆ send data to BCD display
  - signal `data_out` – temperature in °F or °C
  - signal `F/C BCD` – display temperature scale
- ◆ repeat steps for new temperature input



## VHDL description

- ◆ describe FSM as a separate entity
- ◆ integrate all components of the system using structural VHDL
- ◆ VHDL components reference existing designs
  - ALU
  - register file
  - FSM
- ◆ implement required glue logic in the VHDL net list



## Complete the following tasks

- ◆ design the control unit for this design as FSM in VHDL
- ◆ integrate all components in a single design
- ◆ simulate the design to validate functionality
- ◆ synthesize the design
- ◆ simulate synthesis results

