

# PART 7

## Synthesis

- **Main concepts**
- **Structural synthesis**
- **Combinational circuits**
- **Functional registers**
- **State machines**

**In general:**

**We will present an overview of synthesis. What is expected from present tools.**

## Synthesis.main\_concepts

Hardware Generation

Library Mapping


Optimization

Resource sharing



- Synthesis transforms one hardware format to another
- Results are mapped to a certain library
- Optimization reduces logic
- Resources such as adders can be reused

## Synthesis.main\_concepts

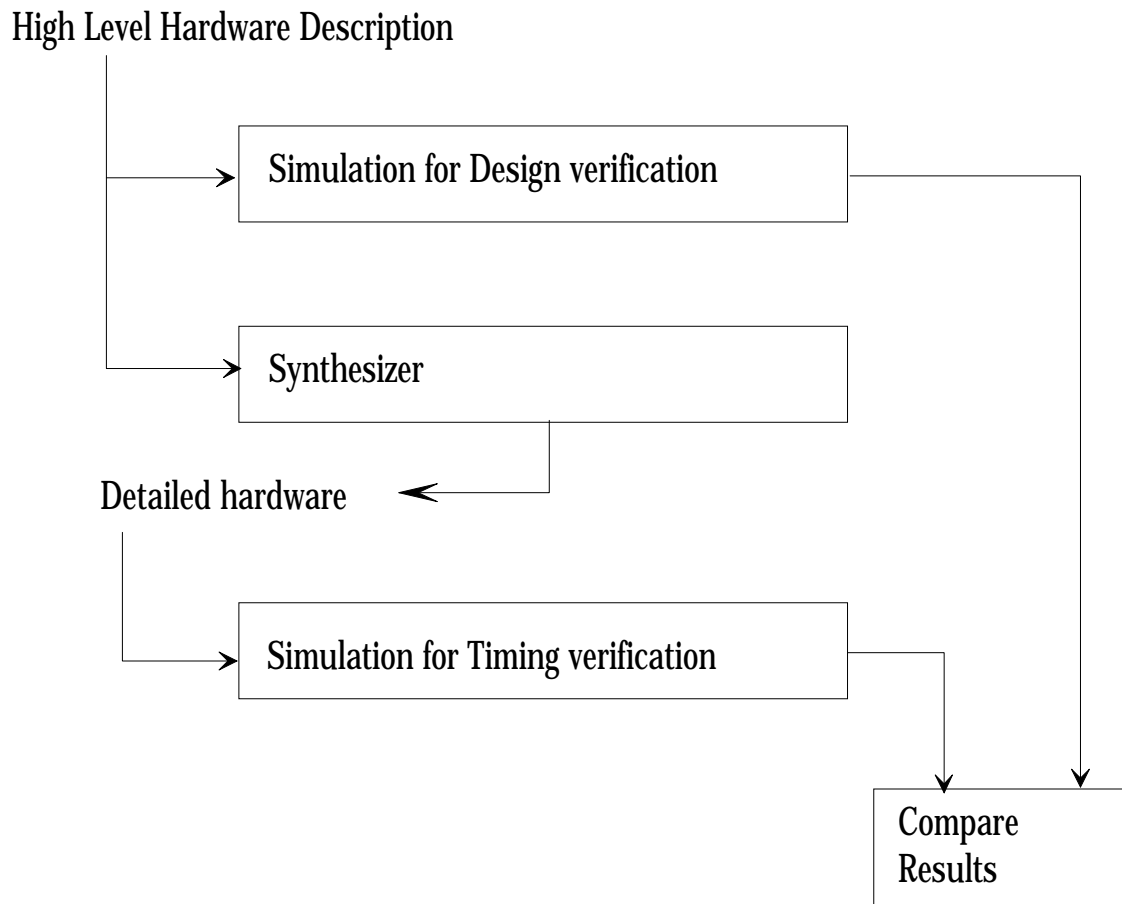

- Design process includes high level simulation
- Synthesizer is used after design verification
- Simulate after synthesis to verify timing

## Synthesis.main\_concepts

Std\_logic

Integer

Enumeration types



- Synthesizers support IEEE 1164 mv19
- Integer type for signals is supported
- Enumeration types are used for states of state machines
- No timing of type TIME is synthesized

## Synthesis.main\_concepts

### Can synthesize

Structural

Dataflow

Behavioral



- Can start with *sub\_component* specification
- Can use signal assignments
- Can specify functionality in a process statement

## Synthesis.main\_concepts

```
ARCHITECTURE structural OF xnor IS
  COMPONENT xor2 PORT ( i1, i2 : IN BIT; o1 : OUT BIT );
  COMPONENT not1 PORT ( i1 : IN BIT; o1 : OUT BIT );
  SIGNAL x : BIT;
BEGIN
  c1 : xor2 PORT MAP ( i1, i2, x );
  c2 : not1 PORT MAP ( x, o1 );
END structural;
```



- At the structural level, wiring predefined parts are specified
- Parts come from specific technology libraries

## Synthesis.main\_concepts

```
ARCHITECTURE dataflow OF xnor IS  
BEGIN  
  o1 <= NOT (i1 XOR i2);  
END dataflow;
```



- Dataflow specifies bus and register transfers
- Synthesizers generate hardware specified at dataflow level

## Synthesis.main\_concepts

```
ARCHITECTURE behavioral OF xnor IS
BEGIN
  PROCESS ( i1, i2 )
  BEGIN
    IF i1 = i2 THEN
      o1 <= '1';
    ELSE
      o1 <= '0';
    END IF;
  END PROCESS
END behavioral
```



- Behavioral level is the easiest to specify hardware
- Synthesizers use this level for synthesis
- Certain rules must be followed


## Synthesis.structural\_synthesis

```
ARCHITECTURE structural OF counter2 IS
  COMPONENT dff PORT(ck, data : IN BIT; q : OUT BIT);
  END COMPONENT;
  COMPONENT xor2 PORT (i1, i2 : IN BIT; o1 : OUT BIT);
  END COMPONENT;
  COMPONENT not1 PORT (i1 : IN BIT ; o1 : OUT BIT);
  END COMPONENT;
  SIGNAL d1, y, d0, y0 : BIT;
BEGIN
  u1 : dff  PORT MAP (clk, d1, y1);
  u2 : dff  PORT MAP (clk, d0, y0);
  u3 : xor2 PORT MAP (y1, y0, d1);
  u4 : not1 PORT MAP (y0, d0);
  count0 <= y0;
  count1 <= y1;
END structural;
```



- Use structural to build larger components from smaller ones
- Can wire full adders into *n\_bit* adders
- Hardware is generated from predefined library cells

## Synthesis.structural\_synthesis

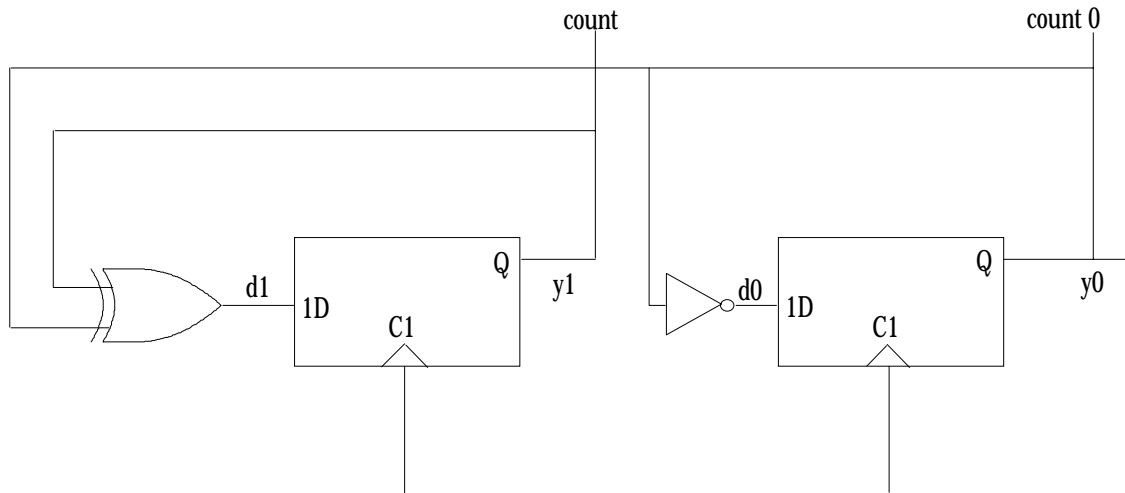


- Hardware generated from structural of counter2
- Can use this design in larger designs
- Can do other parts of design at dataflow or structural
- This way you control parts to use
- Some libraries may include large functional blocks
- Structural synthesis allows use of functional blocks

## Synthesis.combinational\_circuits

```

ENTITY selecting IS
  PORT (a, select_a, b, select_b, c : IN std_logic; z : OUT std_logic);
END selecting;
ARCHITECTURE behavioral OF selecting IS
BEGIN
  PROCESS (a, select_a, b, select_b, c)
  BEGIN
    IF select_a = '1' THEN
      z <= a;
    ELSIF select_b = '1' THEN
      z <= b;
    ELSE
      z <= c;
    END IF;
  END PROCESS;
END behavioral;

```

 

- A behavioral combinational process translates to a combinational circuit
- Process must be sensitive to all inputs
- This process does not store values

## Synthesis.combinational\_circuits

```
ARCHITECTURE dataflow OF selecting IS  
BEGIN  
    z <= a WHEN select_a = '1' ELSE  
        b WHEN select_b = '1' ELSE  
        c;  
END dataflow;
```




- Same hardware can be generated by a dataflow description
- In this description AFTER clauses are ignored by the synthesizer
- Can use subprograms for logic functions

## Synthesis.combinational\_circuits

```

.
.
.
bus_a <= reg_1 WHEN put_reg_1_on_bus = '1'
      ELSE "zzzz";
.
.
.
bus_a <= reg_z WHEN put_reg_z_on_bus = '1'
      ELSE "zzzz";
.
.
.

```

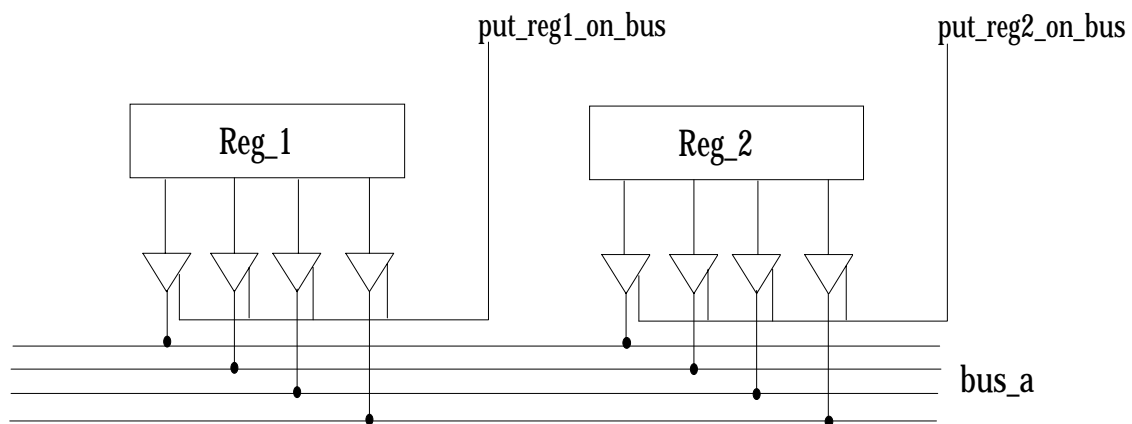

- Bussing can be specified by use of conditional signal assignments
- Assigning "zzzz" is synthesized as opening a *three\_state* gate
- Hardware is generated by use of available library cells


## Synthesis.functional\_registers

```
ENTITY counter2 IS
    PORT (clk, reset : IN std_logic;
          count : BUFFER std_logic_vector ( 1 DOWNTO 0));
END counter2;
--
ARCHITECTURE behavioral OF counter2 IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL ( clk'EVENT AND clk = '1' );
        IF reset = '1' OR count = "11" THEN
            count <= "00";
        ELSE
            count <= count + "01";
        END IF;
    END PROCESS;
END behavioral;
```



- A WAIT in process, implies clocking
- Can also use IF( clk' EVENT AND clk = '1') with sensitivity list
- An edge condition must be the last of IF statement

## Synthesis.functional\_registers

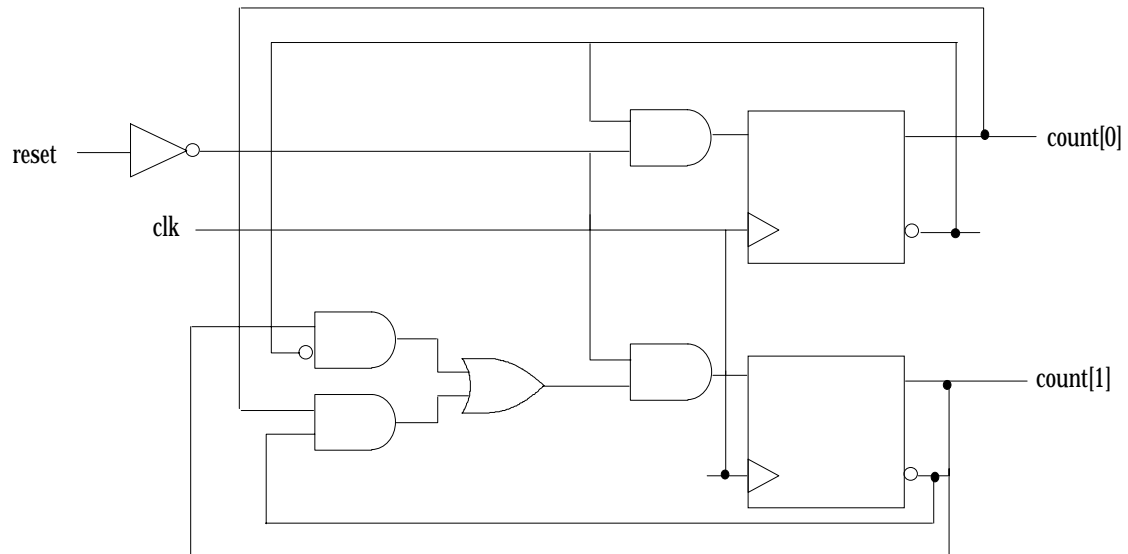

- A possible hardware generated for counter
- Cells from an available library are used




## Synthesis.functional\_registers

```
ARCHITECTURE dataflow OF counter2 IS
BEGIN
  bc : BLOCK ( clk'EVENT AND clk = '1' )
  BEGIN
    count <= GUARDED '00' WHEN reset = '1' ELSE
    count +"01";
  END BLOCK;
END dataflow;
```





- Can also synthesize dataflow descriptions
- A guarded block specifies clocking
- Generates same hardware as behavioral descriptions

## Synthesis.state\_machines

   

- 
- State machines describe general hardware
  - A simple state machine assigns values to outputs
  - Synthesizers take state machines with programs with flow instead of simple output values
  - Can use high level constructs for such programs

## Synthesis.state\_machines

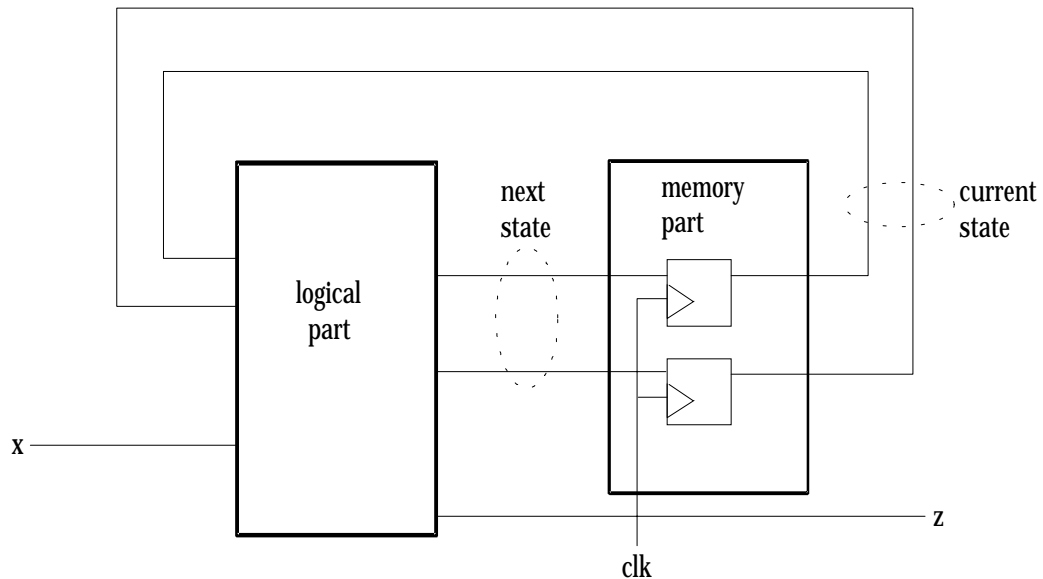 

- Can describe state machines with logical and memory parts
- Logical part defines sequencing
- Memory part updates current state with clock

## Synthesis.state\_machines

```

ENTITY detector IS
  PORT ( x, clk : IN std_logic; z : OUT std_logic);
END detector;
---
ARCHITECTURE behavioral OF detector IS
  TYPE state IS ( reset, got1, got11, got110 );
  SIGNAL next_state, current_state : states;
BEGIN
  sequencing : PROCESS ( current_state, x )
  BEGIN
    z <= '0';
    CASE current_state IS
      WHEN reset =>
        IF x = '0' THEN next_state <= reset; ELSE next_state <= got1;
        END IF;
      WHEN got1 =>
        IF x = 0 THEN next_state <= reset; ELSE next_state <= got11;
        END IF;
      WHEN got11 =>
        IF x = 0 THEN next_state <= got110; ELSE next_state <= got11;
        END IF;
      WHEN got110;
        z <= '1';
        IF x = 0 THEN next_state <= reset; ELSE next_state <= got1;
        END IF;
    END CASE;
  END PROCESS;
  clocking : PROCESS ( clk )
  BEGIN
    IF ( clk'EVENT AND clk = '0' ) THEN
      CURRENT_STATE <= NEXT_STATE;
    END IF;
  END PROCESS;
END behavioral;

```

- Sequencing PROCESS for logical part
- Clocking PROCESS for memory part

## Synthesis.state\_machines

### Hardware design

1. Design state machine  
use programs between states  
use CASE, IF\_THEN, ... for assigning output values
2. Partition into data and control  
synthesize data units  
synthesize control unit by a state machine



- Two design methods both use state machine descriptions
- Next two parts will present these methods

## Synthesis.conclusions

**1. Outline:** Introduction, Organization, Outline

**2. Review:** Levels of abstraction, Entity and Architecture, Signal assignments, Guarded signal assignments, Three state bussing, Process statements, Combinational processes, Sequential processes, Multiplexing, Package

**3. MSI Based Design:** Use MSI parts of Part 2, Sequential multiplication, Designing the multiplier, Control and data parts, Testing the multiplier

**4. General CPU Description:** Will present a high level VHDL description of a small CPU. The CPU, Memory organization, Instructions, Addressing, Utilities for VHDL description, Interface, Behavioral description, Coding individual instructions

**5. Manual Data\_path Design:** Will present VHDL description for manual design of data\_path. Data components, Bussing structure, Description of logic, Description of registers, Bus resolutions, Component wiring

**6. Manual Controller Design:** Will present VHDL description for manual design of controller. Controller hardware, VHDL style, Signals and resolutions, State descriptions, Complete CPU, Testing CPU

<p><b>7. Synthesis:</b> Main concepts, Structural synthesis, Combinational circuits, Functional registers, State machines</p>
---

**8. Behavioral\_Synthesis:** Will present a high level synthesizable CPU description. Synthesis style, Necessary Package, Interface, General Layout, Registers, Clocking, Sequencing, Simulation and Synthesis

**9. Dataflow\_Synthesis:** Will partition the CPU and synthesize each part separately. Synthesis style, Controller, Data components, Data path, Synthesized example, Conclusions